

Numbers

Every number system is associated with a base or radix

A positional notation is commonly used to express numbers

$$(a_5a_4a_3a_2a_1a_0)_r = a_5r^5 + a_4r^4 + a_3r^3 + a_2r^2 + a_1r^1 + a_0r^0$$

The decimal system has a base of 10 and uses symbols (0,1,2,3,4,5,6,7,8,9) to represent numbers

$$(2009)_{10} = 2 \times 10^3 + 0 \times 10^2 + 0 \times 10^1 + 9 \times 10^0$$

$$(123.24)_{10} = 1 \times 10^2 + 2 \times 10^1 + 3 \times 10^0 + 2 \times 10^{-1} + 4 \times 10^{-2}$$

An octal number system has a base 8 and uses symbols (0,1,2,3,4,5,6,7)

$$(2007)_8 = 2 \times 8^3 + 0 \times 8^2 + 0 \times 8^1 + 7 \times 8^0$$

What decimal number does it represent?

$$(2007)_8 = 2 \times 512 + 0 \times 64 + 0 \times 8^1 + 7 \times 8^0 = 1033$$

A hexadecimal system has a base of 16

Number	Symbol
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	A
11	B
12	C
13	D
14	E
15	F

$$(2BC9)_{10} = 2 \times 16^3 + B \times 16^2 + C \times 16^1 + 9 \times 16^0$$

How do we convert it into decimal number?


$$(2BC9)_{10} = 2 \times 4096 + 11 \times 256 + 12 \times 16^1 + 9 \times 16^0 = 11209$$

A Binary system has a base 2 and uses only two symbols 0, 1 to represent all the numbers

$$(1101)_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

Which decimal number does this correspond to ?
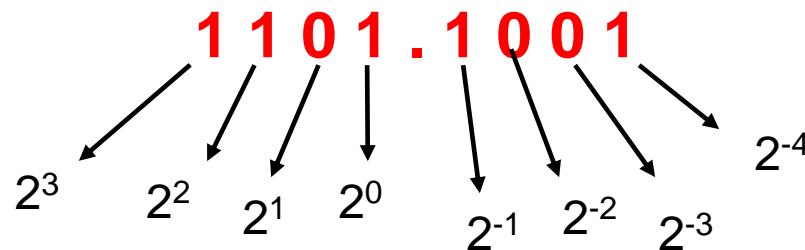
$$(1101)_2 = 1 \times 8 + 1 \times 4 + 0 \times 2^1 + 1 \times 2^0 = 13$$



2^0	1
2^1	2
2^2	4
2^3	8
2^4	16
2^5	32
2^6	64
2^7	128
2^8	256
2^9	512
2^{10}	1024(K)
2^{20}	1048576(M)

2^{-1}	2^{-2}	2^{-3}	2^{-4}	2^{-5}	2^{-6}
0.5	0.25	0.125	0.0625	0.03125	0.015625

Developing Fluency with Binary Numbers

$$1\ 1\ 0\ 0\ 1 = ?$$

$$25$$

$$1100001 = ?$$

$$64+32+1=97$$

$$0.101 = ?$$

$$0.5+0.125=0.625$$

$$11.001 = ?$$

$$3+0.125=3.125$$

Converting decimal to binary number

Convert 45 to binary number

$$(45)_{10} = b_n b_{n-1} \dots b_0$$

$$45 = b_n 2^n + b_{n-1} 2^{n-1} \dots b_1 2^1 + b_0$$

Divide both sides by 2

$$\frac{45}{2} = 22.5 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots b_1 2^0 + b_0 \times 0.5$$

$$22 + 0.5 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots + b_1 2^0 + b_0 \times 0.5$$

$$\Rightarrow b_0 = 1$$

$$22 + 0.5 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots + b_1 2^0 + b_0 \times 0.5 \quad \Rightarrow b_0 = 1$$

$$22 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots b_2 2^1 + b_1 2^0$$

Divide both sides by 2

$$\frac{22}{2} = 11 = b_n 2^{n-2} + b_{n-1} 2^{n-3} \dots b_2 2^0 + b_1 \times 0.5 \quad \Rightarrow b_1 = 0$$

$$11 = b_n 2^{n-2} + b_{n-1} 2^{n-3} \dots + b_3 2^1 + b_2 2^0$$

$$5.5 = b_n 2^{n-3} + b_{n-1} 2^{n-4} \dots + b_3 2^0 + 0.5 b_2 \quad \Rightarrow b_2 = 1$$

$$5 = b_n 2^{n-3} + b_{n-1} 2^{n-4} \dots b_4 2^1 + b_3 2^0$$

$$5 = b_n 2^{n-3} + b_{n-1} 2^{n-4} \dots b_4 2^1 + b_3 2^0$$

$$2.5 = b_n 2^{n-4} + b_{n-1} 2^{n-5} \dots b_4 2^0 + 0.5b_3 \Rightarrow b_3 = 1$$

$$2 = b_n 2^{n-4} + b_{n-1} 2^{n-5} \dots b_5 2^1 + b_4 2^0$$

$$1 = b_n 2^{n-5} + b_{n-1} 2^{n-6} \dots b_5 2^0 + 0.5b_4 \Rightarrow b_4 = 0$$

$$\Rightarrow b_5 = 1$$

$$(45)_{10} = b_5 b_4 b_3 b_2 b_1 b_0 = 101101$$

Converting decimal to binary number

Method of successive division by 2

45	remainder
22	1
11	0
5	1
2	1
1	0
0	1

45 = 1 0 1 1 0 1

The diagram illustrates the conversion of the decimal number 45 to its binary equivalent, 101101, using the method of successive division by 2. A table shows the sequence of divisions and the resulting remainders. Red arrows indicate that the remainders are read from the bottom of the table to the top to form the binary number. The final result is shown as 45 = 1 0 1 1 0 1.

Convert $(153)_{10}$ to octal number system

$$(153)_{10} = (b_n b_{n-1} \dots b_0)_8$$

$$(153)_{10} = b_n 8^n + b_{n-1} 8^{n-1} \dots b_1 8^1 + b_0$$

Divide both sides by 8

$$\frac{153}{8} = 19.125 = b_n 8^{n-1} + b_{n-1} 8^{n-2} \dots b_1 8^0 + \frac{b_0}{8} \Rightarrow \frac{b_0}{8} = 0.125 \Rightarrow b_0 = 1$$

153	remainder
19	1
2	3
0	2

$$153 = (231)_8$$

Converting decimal to binary number

Convert $(0.35)_{10}$ to binary number

$$(0.35)_{10} = 0.b_{-1}b_{-2}b_{-3}\dots\dots b_{-n}$$

$$0.35 = 0 + b_{-1}2^{-1} + b_{-2}2^{-2} + \dots\dots b_{-n}2^{-n}$$

How do we find the b_{-1} b_{-2} ...coefficients?

Multiply both sides by 2

$$0.7 = b_{-1} + b_{-2}2^{-1} + \dots\dots b_{-n}2^{-n+1} \quad \Rightarrow b_{-1} = 0$$

$$0.7 = b_{-2}2^{-1} + b_{-3}2^{-2} + \dots\dots b_{-n}2^{-n+1}$$

$$0.7 = b_{-2}2^{-1} + b_{-3}2^{-2} + \dots b_{-n}2^{-n+1}$$

Multiply both sides by 2

$$1.4 = b_{-2} + b_{-3}2^{-1} + \dots b_{-n}2^{-n+2}$$

Note that $\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \leq 1$ $\Rightarrow b_{-2} = 1$

$$0.4 = b_{-3}2^{-1} + b_{-4}2^{-2} \dots b_{-n}2^{-n+2}$$

$$0.8 = b_{-3} + b_{-4}2^{-1} \dots b_{-n}2^{-n+3} \Rightarrow b_{-3} = 0$$

Converting decimal to binary number

0.125 = ?

0 .	125	
<hr/>		
		x2
0 .	25	
		x2
0 .	5	
		x2
1 .	0	

0.125 = $(.001)_2$

0.8125 = ?

0 .	8125	
<hr/>		
		x2
1 .	625	
		x2
1 .	25	
		x2
0 .	5	
		x2
1 .	0	

0.8125 = $(.1101)_2$

Binary numbers

Most significant bit or **MSB**

Least significant bit or **LSB**

1011000111

This is a 10 bit number

Binary digit = bit

decimal	2bit	3bit	4bit	5bit
0	00	000	0000	00000
1	01	001	0001	00001
2	10	010	0010	00010
3	11	011	0011	00011
4		100	0100	00100
5		101	0101	00101
6		110	0110	00110
7		111	0111	00111
8			1000	01000
9			1001	01001
10			1010	01010
11			1011	01011
12			1100	01100
13			1101	01101
14			1110	01110
15			1111	01111


N-bit binary number can represent numbers from 0 to $2^N - 1$

Converting Binary to Hex and Hex to Binary


$$(b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0)_b = (h_1, h_0)_{Hex}$$

$$b_7 2^7 + b_6 2^6 + b_5 2^5 + b_4 2^4 + b_3 2^3 + b_2 2^2 b_1 2^1 + b_0 = h_1 16^1 + h_0$$
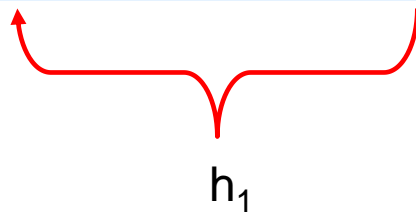
$$(b_7 2^3 + b_6 2^2 + b_5 2^1 + b_4) 2^4 + (b_3 2^3 + b_2 2^2 b_1 2^1 + b_0) = h_1 16^1 + h_0$$



$$h_1$$

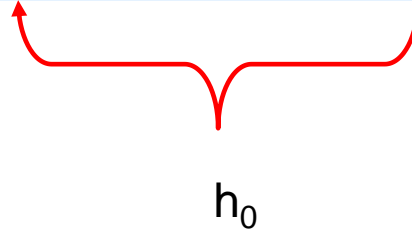

$$h_0$$

$$(10110011)_b = (1011)(0011) = (B3)_{Hex}$$

$$(110011)_b = (11)(0011) = (33)_{Hex}$$

$$(EC)_{Hex} = (1110)(1100) = (11101100)_b$$

Number	Symbol
0(0000)	0
1(0001)	1
2(0010)	2
3(0011)	3
4(0100)	4
5(0101)	5
6(0110)	6
7(0111)	7
8(1000)	8
9(1001)	9
10(1010)	A
11(1011)	B
12(1100)	C
13(1101)	D
14(1110)	E
15(1111)	F

Binary Addition/Subtraction

$$\begin{array}{r} 0 \\ \hline 0 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 1 \\ \hline 0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 1 \\ \hline 1 \end{array}$$


$$\begin{array}{r} 1 \\ \hline 1 \\ \hline 10 \end{array}$$

$$\begin{array}{r} 1 \\ 1 \\ \hline 1 \\ \hline 11 \end{array}$$

$$\begin{array}{r} 101 \\ \hline 110 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 1101 \\ + 1110 \\ \hline 11011 \end{array}$$

Complement of a number

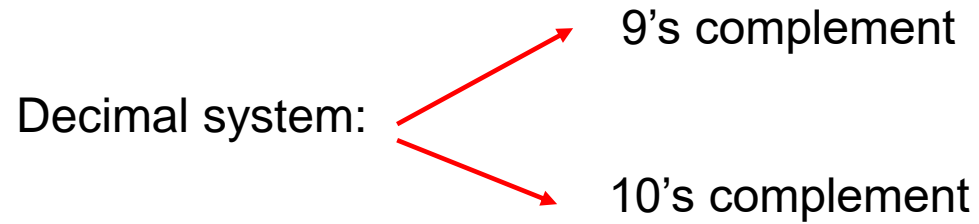

9's complement of n-digit number x is $10^n - 1 - x$


10's complement of n-digit number x is $10^n - x$

9's complement of 85 ? $10^2 - 1 - 85$ $99 - 85 = 14$

$$9's \text{ complement of } 123 = 999 - 123 = 876$$

$$10's \text{ complement of } 123 = 9's \text{ complement of } 123 + 1 = 877$$

Complement of a binary number

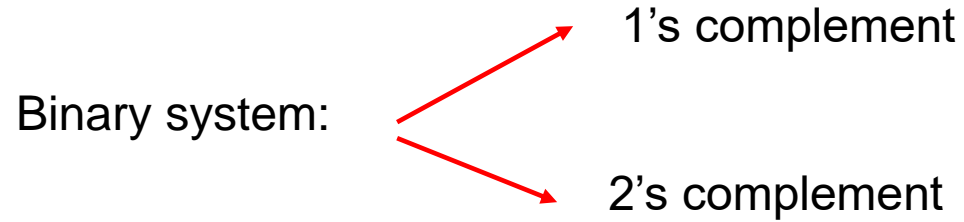

1's complement of n-bit number x is $2^n - 1 - x$

2's complement of n-bit number x is $2^n - x$

1's complement of 1011 ? $2^4 - 1 - 1011$ $1111 - 1011 = 0100$

1's complement is simply obtained by flipping a bit (changing 1 to 0 and 0 to 1)

1's complement of 1001101 = ?

0110010

2's complement of 1010 = 1's complement of 1010 + 1 = 0110

2's complement of 110010 =

Leave all least significant 0's as they are, leave first 1 unchanged and then flip all subsequent bits

001110

1011 → 0101

101101100 → 010010100

Representing positive and negative binary numbers

One extra bit is required to carry sign information. Sign bit = 0 represents positive number and Sign bit = 1 represents negative number

decimal	Signed Magnitude
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
-0	1000
-1	1001
-2	1010
-3	1011
-4	1100
-5	1101
-6	1110
-7	1111


decimal	Signed 1's complement
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
-0	1111
-1	1110
-2	1101
-3	1100
-4	1011
-5	1010
-6	1001
-7	1000

decimal	Signed 2's complement
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001

Boolean Algebra


Algebra on Binary numbers

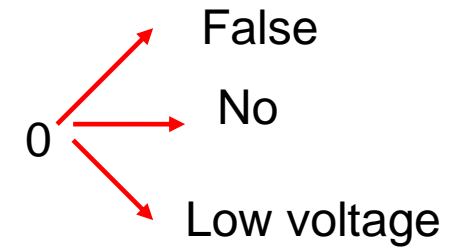A variable x can take two values $\{0,1\}$



Basic operations:

$$\text{AND: } y = x_1 \cdot x_2$$

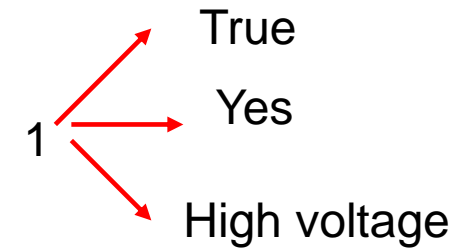

Y is 1 if and only if both x_1 and x_2 are 1, otherwise zero

Truth Table

x_1	x_2	y
0	0	0
0	1	0
1	0	0
1	1	1

Basic operations:

$$\text{OR: } y = x_1 + x_2$$

Y is 1 if either x_1 and x_2 is 1. Or $y = 0$ if and only if both variables are zero

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	1

$$\text{NOT: } y = \bar{x}$$

x	y
0	1
1	0

Boolean Algebra

Basic Postulates

$$P1: \quad x + 0 = x$$

$$P2: \quad x + y = y + x$$

$$P3: \quad x.(y+z) = x.y+x.z$$

$$P4: \quad x + \bar{x} = 1$$

$$P1: \quad x . 1 = x$$

$$P2: \quad x . y = y . x$$

$$P3: \quad x+y.z = (x+y).(x+z)$$

$$P4: \quad x . \bar{x} = 0$$

Basic Theorems

$$T1: \quad x + x = x$$

$$T2: \quad x + 1 = 1$$

$$T3: \quad \overline{(\bar{x})} = x$$

$$T4: \quad x + (y+z) = (x+y)+z$$

$$T5: \quad \overline{(x+y)} = \bar{x} . \bar{y} \text{ (DeMorgan's theorem)}$$

$$T6: \quad x + x.y = x$$

$$T1: \quad x . x = x$$

$$T2: \quad x . 0 = 0$$

$$T4: \quad x . (y.z) = (x.y).z$$

$$T5: \quad \overline{(x.y)} = \bar{x} + \bar{y} \text{ (DeMorgan's theorem)}$$

$$T6: \quad x.(x+y) = x$$

Proving theorems

$$P1: \quad x + 0 = x$$

$$P2: \quad x + y = y + x$$

$$P3: \quad x.(y+z) = x.y+x.z$$

$$P4: \quad x + \bar{x} = 1$$

$$P1: \quad x . 1 = x$$

$$P2: \quad x . y = y . x$$

$$P3: \quad x+y.z = (x+y).(x+z)$$

$$P4: \quad x . \bar{x} = 0$$

$$\text{Prove T1: } x + x = x$$

$$x + x = (x+x). 1 \text{ (P1)}$$

$$= (x+x). (x+\bar{x}) \text{ (P4)}$$

$$= x + x.\bar{x} \text{ (P3)}$$

$$= x + 0 \text{ (P4)}$$

$$= x \text{ (P1)}$$

$$\text{Prove T1: } x . x = x$$

$$x . x = x.x+ 0 \text{ (P1)}$$

$$= x.x + x.\bar{x} \text{ (P4)}$$

$$= x . (x+\bar{x}) \text{ (P3)}$$

$$= x . 1 \text{ (P4)}$$

$$= x \text{ (P1)}$$

Proving theorems

$$P1: x + 0 = x$$

$$P2: x + y = y + x$$

$$P3: x.(y+z) = x.y+x.z$$

$$P4: x + \bar{x} = 1$$

$$P1: x . 1 = x$$

$$P2: x . y = y . x$$

$$P3: x+y.z = (x+y).(x+z)$$

$$P4: x . \bar{x} = 0$$

$$\text{Prove : } x + 1 = 1$$

$$x + 1 = x + (x + \bar{x})$$

$$= (x+x) + \bar{x}$$

$$= x + \bar{x}$$

$$= 1$$

$$x + x . y = x$$

$$= x . 1 + x . y$$

$$= x . (1 + y)$$

$$= x . 1$$

$$= x$$

$$x + \bar{x} . y = x + y$$

$$= (x + \bar{x}) . (x + y)$$

$$= 1 . (x + y)$$

$$= x + y$$

DeMorgan's theorem

$$\overline{(x_1 + x_2 + x_3 + \dots)} = \bar{x}_1 . \bar{x}_2 . \bar{x}_3 .$$

$$\overline{(x_1 . x_2 . x_3 \dots)} = (\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \dots)$$

Simplification of Boolean expressions

$$\overline{(\overline{X_1} \cdot X_2 + \overline{X_2} \cdot X_3)} = ?$$



$$\overline{(X_1 + X_2 + X_3 + \dots)} = \overline{X_1} \cdot \overline{X_2} \cdot \overline{X_3} \cdot$$

$$\overline{(X_1 \cdot X_2 \cdot X_3 \dots)} = (\overline{X_1} + \overline{X_2} + \overline{X_3} + \dots)$$

$$= (X_1 + \overline{X_2}) \cdot (X_2 + \overline{X_3})$$

$$= X_1 \cdot X_2 + X_1 \cdot \overline{X_3} + \overline{X_2} \cdot \overline{X_3}$$

Function of Boolean variables

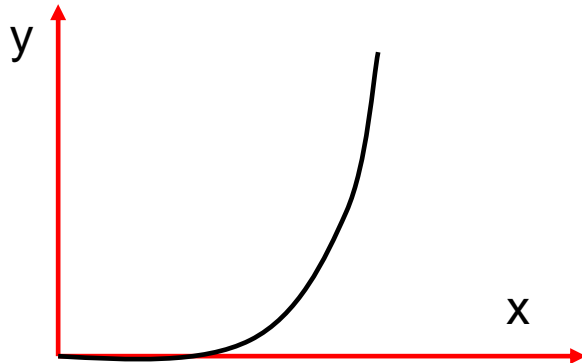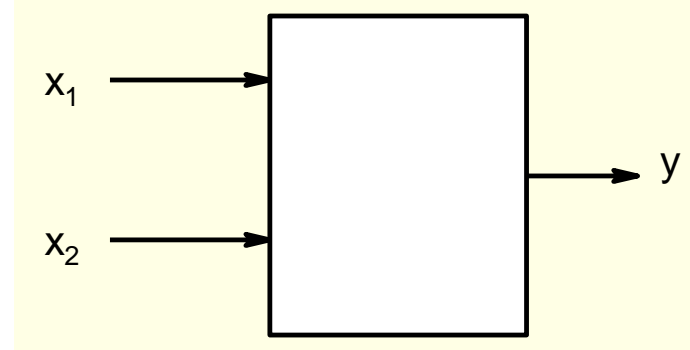

$$y = x^2$$

x_1	x_2	y
0	0	0
0	1	1
1	0	0
1	1	0

$Y = 1$ when x_1 is 0 and x_2 is 1

$$y = \overline{x_1} \cdot x_2$$

Boolean expression

Obtaining Boolean expressions from truth Table

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2}$$

x_1	x_2	y
0	0	0
0	1	0
1	0	1
1	1	0

$$y = x_1 \cdot \overline{x_2}$$

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{x_1} \cdot \overline{x_2}$$

$$x_1 \cdot x_2$$

$$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

Obtaining Boolean expressions from truth Table

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

Instead of writing expressions as sum of terms that make y equal to 1, we can also write expressions using terms that make y equal to 0

x_1	x_2	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2} + \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

$$y = \overline{x_1} + \overline{x_2}$$

x_1	x_2	y
0	0	1
0	1	0
1	0	1
1	1	1

$$y = x_1 + \overline{x_2}$$

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	1

$$y = x_1 + x_2$$

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$x_1 + x_2$$

$$y = (x_1 + x_2) \cdot (\overline{x_1} + \overline{x_2})$$

$$\overline{x_1} + \overline{x_2}$$

Obtaining Boolean expressions from truth Table

x_1	x_2	x_3	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

Sum of Products (SOP) form

$$y = (x_1 + x_2 + x_3) \cdot (x_1 + \overline{x_2} + x_3) \cdot (\overline{x_1} + x_2 + x_3) \cdot (\overline{x_1} + \overline{x_2} + x_3)$$

Product of Sum (POS) form

Obtaining Boolean expressions from truth Table

x_1	x_2	x_3	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

Sum of Products (SOP) form


$$y = (x_1 + x_2 + x_3) \cdot (x_1 + \overline{x_2} + x_3) \cdot (\overline{x_1} + x_2 + x_3) \cdot (\overline{x_1} + \overline{x_2} + x_3)$$

Product of Sum (POS) form



Implementing Boolean expressions

Elementary Gates


$$\text{AND: } y = x_1 \cdot x_2$$

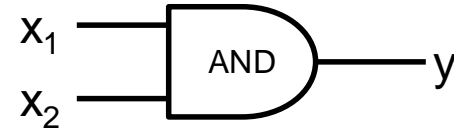

Why call it a gate?

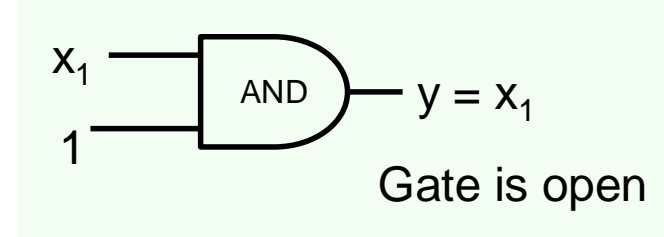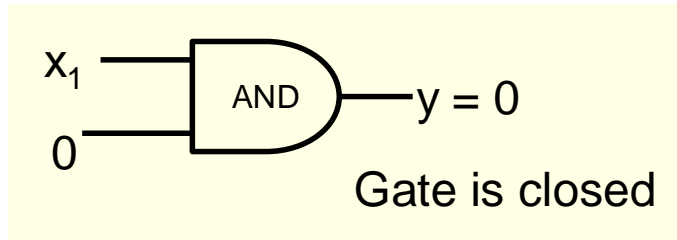


$$\text{OR: } y = x_1 + x_2$$

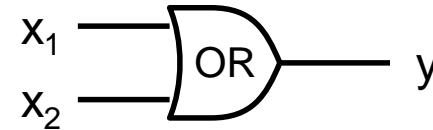



$$\text{NOT: } y = \bar{x}$$



NAND: $y = \overline{x_1 \cdot x_2}$

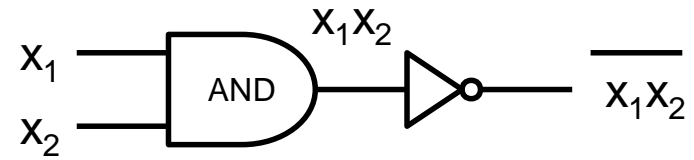



NOR: $y = \overline{x_1 + x_2}$

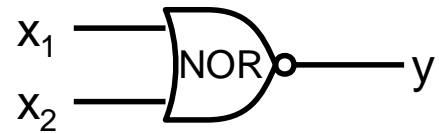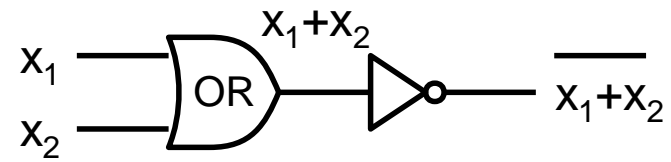

$$\text{XOR: } y = x_1 \oplus x_2 = x_1 \cdot \overline{x_2} + \overline{x_1} \cdot x_2$$


Y is 1 if only one variable is 1 and the other is zero

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

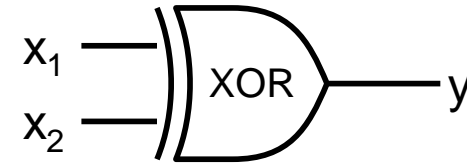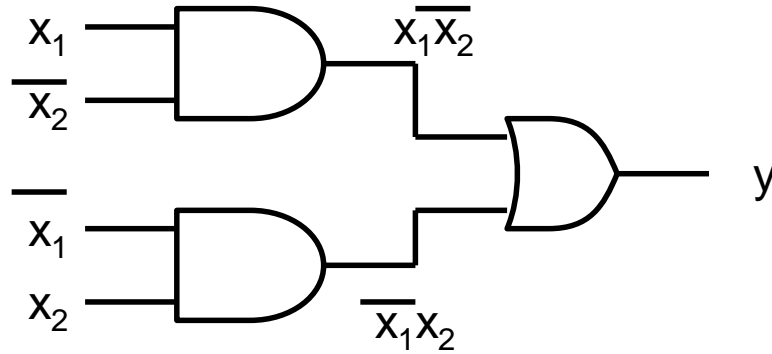

$$\text{XNOR: } y = x_1 \boxdot x_2 = x_1 \cdot x_2 + \overline{x_1} \cdot \overline{x_2}$$

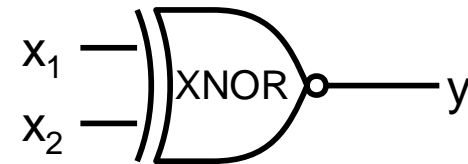
Y is 1 if only both variables are either 0 or 1




$$y = x_1 \boxdot x_2 = \overline{x_1 \oplus x_2}$$

Gates with more than 2 inputs

AND: $y = x_1 \cdot x_2 \cdot x_3 \dots$

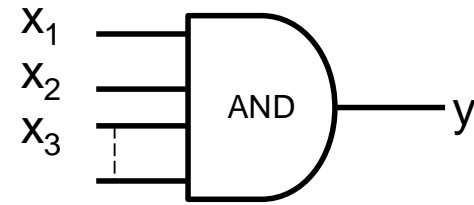


OR: $y = x_1 + x_2 + x_3 + \dots$

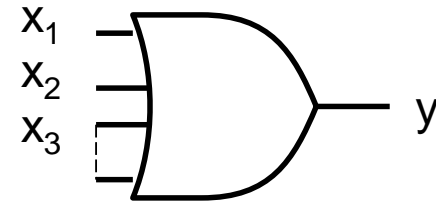

XOR: $y = x_1 \oplus x_2 \oplus x_3 = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot \overline{x_3} + \overline{x_1} \cdot \overline{x_2} \cdot \overline{x_3} + x_1 \cdot x_2 \cdot x_3$



$Y = 1$ only if odd number of inputs is 1

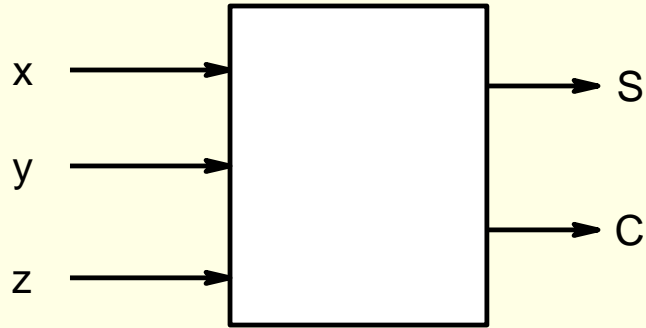Implementing Boolean expressions using gates



$$S = \bar{x}.\bar{y}.z + \bar{x}.y.\bar{z} + x.\bar{y}.\bar{z} + x.y.z$$

$$C = x.y + x.z + y.z$$

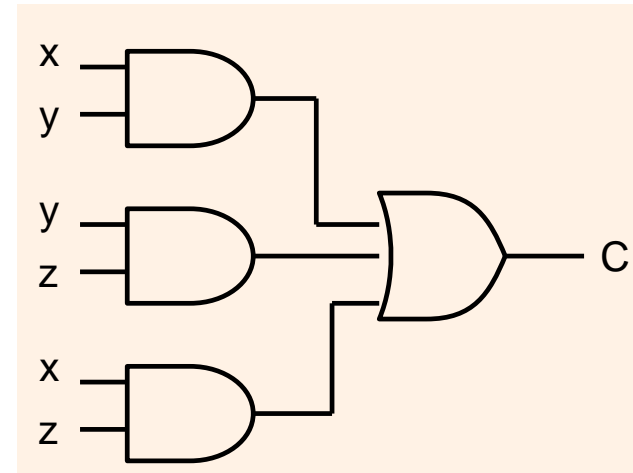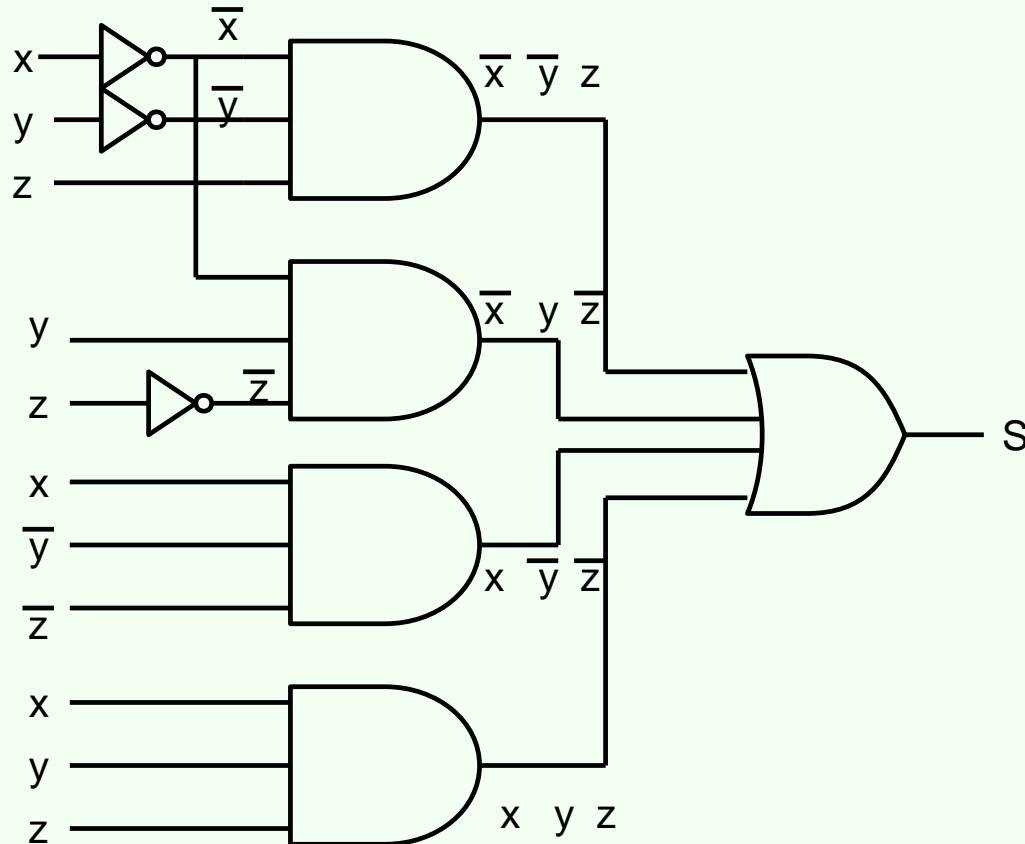


Design Overview






a	b	c	S	CY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
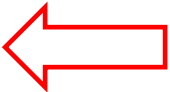
$$S = \overline{x}.\overline{y}.z + \overline{x}.y.\overline{z} + x.\overline{y}.\overline{z} + x.y.z$$



$$C = x.y + x.z + y.z$$

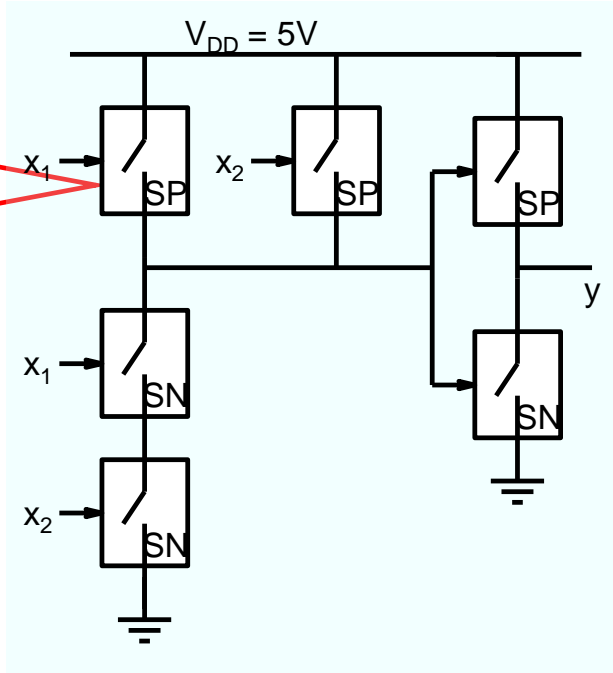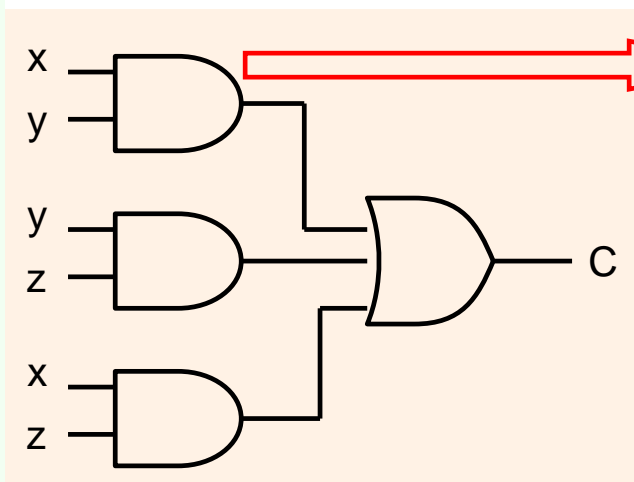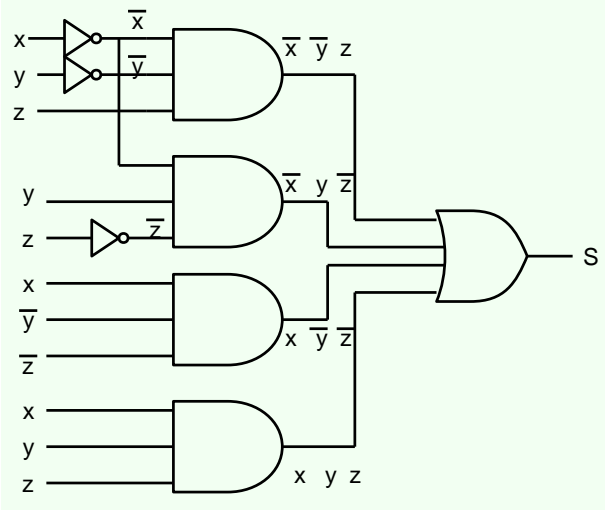

Representation of Boolean Expressions

x	y	f_1
0	0	0
0	1	1
1	0	1
1	1	0

$$f_1 = \bar{x} \cdot y + x \cdot \bar{y}$$

x	y	min term
0	0	$\bar{x} \cdot \bar{y}$ m0
0	1	$\bar{x} \cdot y$ m1
1	0	$x \cdot \bar{y}$ m2
1	1	$x \cdot y$ m3

$$f_1 = m_1 + m_2$$

$$f_1 = \sum (1, 2)$$

$$f_2 = \sum (0, 2, 3) = ?$$

$$f_2 = \bar{x} \cdot \bar{y} + x \cdot \bar{y} + x \cdot y$$

A minterm is a product that contains all the variables used in a function

Three variable functions

x	y	z	min terms	
0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$	m0
0	0	1	$\bar{x} \cdot \bar{y} \cdot z$	m1
0	1	0	$\bar{x} \cdot y \cdot \bar{z}$	m2
0	1	1	$\bar{x} \cdot y \cdot z$	m3
1	0	0	$x \cdot \bar{y} \cdot \bar{z}$	m4
1	0	1	$x \cdot \bar{y} \cdot z$	m5
1	1	0	$x \cdot y \cdot \bar{z}$	m6
1	1	1	$x \cdot y \cdot z$	m7

$$f_2 = \sum (1, 4, 7) = ?$$

$$f_2 = \bar{x} \cdot \bar{y} \cdot z + x \cdot \bar{y} \cdot \bar{z} + x \cdot y \cdot z$$

Product of Sum Terms Representation

x	y	f_1
0	0	1
0	1	0
1	0	0
1	1	1

$$f_1 = (x + \bar{y}).(\bar{x} + y)$$

x	y	Max term
0	0	$x + \underline{y}$ M0
0	1	$\underline{x} + y$ M1
1	0	$\underline{x} + \underline{y}$ M2
1	1	$x + y$ M3

$$f_1 = M_1.M_2$$

$$f_1 = \Pi(1, 2)$$

$$f_2 = \Pi(0, 3) = ?$$

$$f_2 = (x + y).(\bar{x} + \bar{y})$$

x	y	z	Max. terms
0	0	0	$x + y + z$ M0
0	0	1	$x + y + \bar{z}$ M1
0	1	0	$x + \bar{y} + z$ M2
0	1	1	$x + \bar{y} + \bar{z}$ M3
1	0	0	$\bar{x} + y + z$ M4
1	0	1	$\bar{x} + y + \bar{z}$ M5
1	1	0	$\bar{x} + \bar{y} + z$ M6
1	1	1	$\bar{x} + \bar{y} + \bar{z}$ M7

$$f_1 = \Pi(1, 5, 7) = ?$$


$$f_2 = (x + y + \bar{z}).(\bar{x} + y + \bar{z}).(\bar{x} + \bar{y} + \bar{z})$$

Simplification

x_1	x_2	x_3	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$y = \sum (1, 3, 5, 7)$$

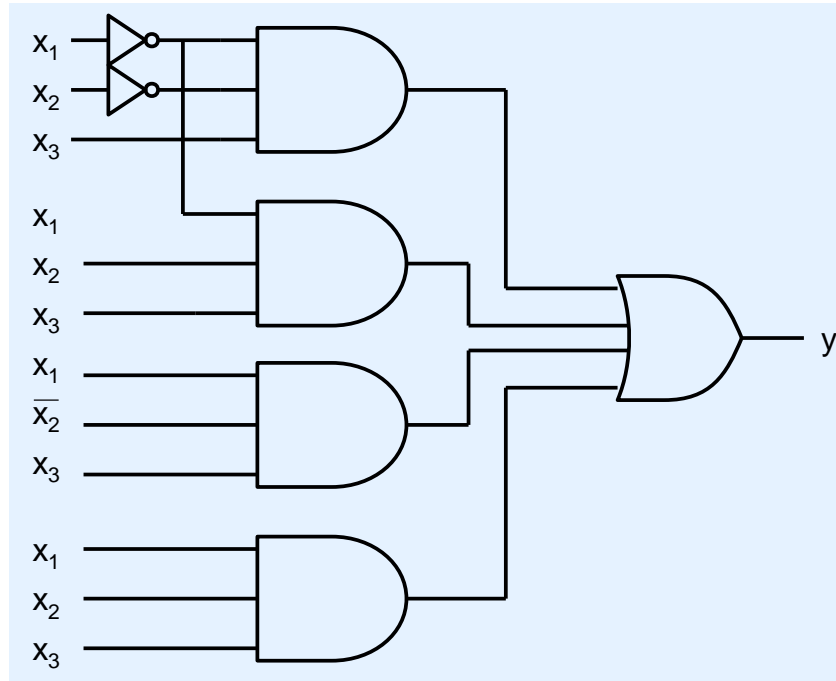
$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



Simplification of Boolean expression yields : $y = x_3$!! which does not require any gates at all !

Goal of Simplification


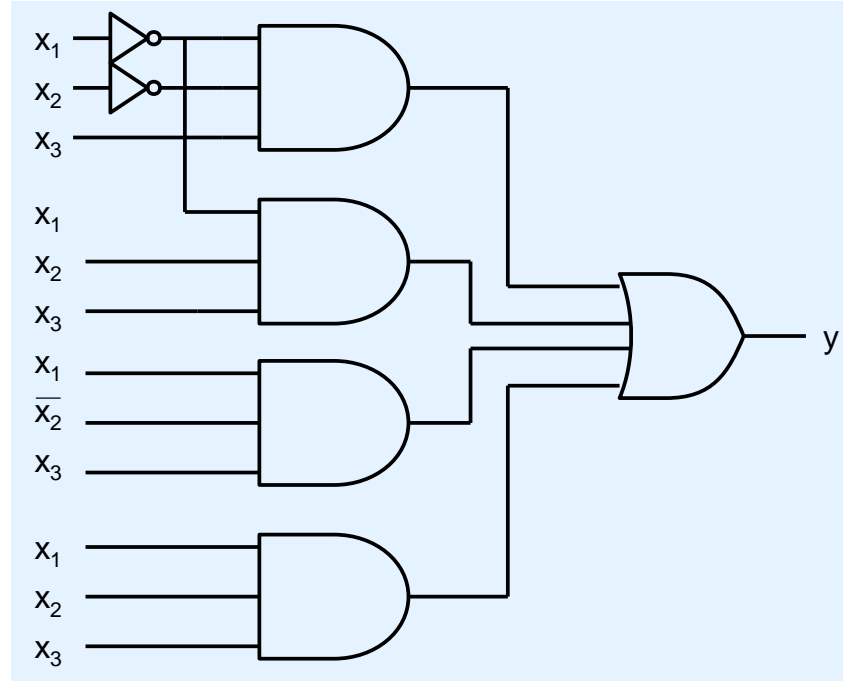
$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$




Goal of simplification is to reduce the complexity of gate circuit. This requires that we minimize the number of gates. Since number of gates depends on number of minterms, one of the goals of simplification is to **minimize the number of minterms in SOP expression**

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot \overline{x_3}$$
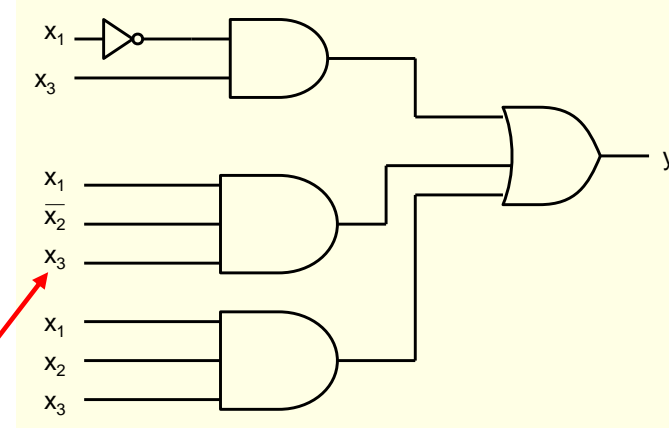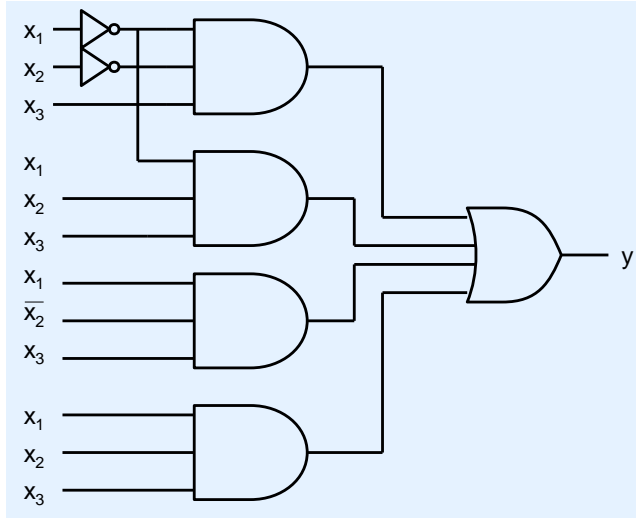
$$\Rightarrow y = \overline{x_1} \cdot x_3 + \overline{x_1} \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



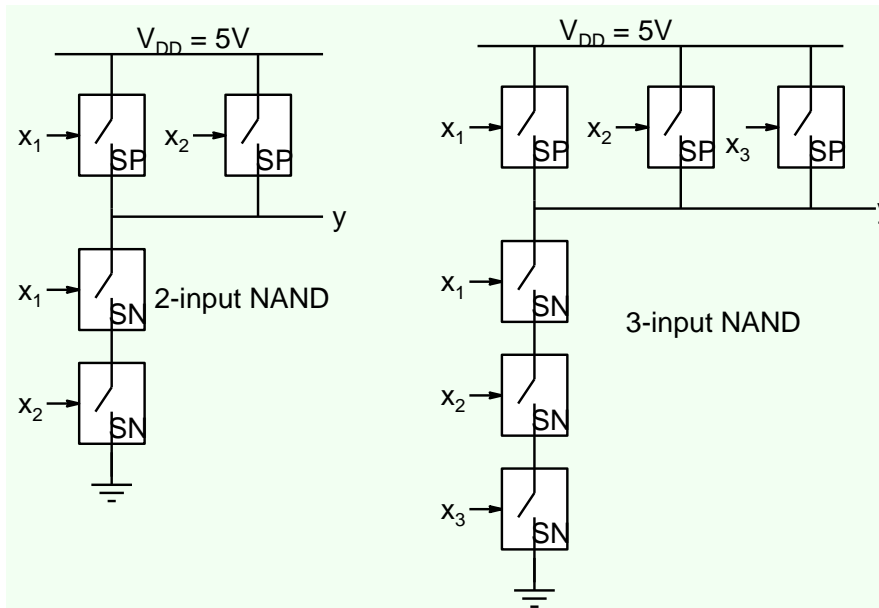This circuit is simpler not just because it uses 4 gates instead of 5 but also because circuit-2 uses one 2-input and three 3-input gates as compared to five 3-input gates used in circuit-1



Goal of Simplification

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

$$\Rightarrow y = \overline{x_1} \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

In the SOP expression:

1. Minimize number of product terms
2. Minimize number of literals in each term

Simplification \Rightarrow Minimization

Minimization

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

$$y = \overline{x_1} \cdot x_3 \cdot (\overline{x_2} + x_2) + x_1 \cdot x_3 \cdot (\overline{x_2} + x_2)$$

$$y = \overline{x_1} \cdot x_3 + x_1 \cdot x_3$$

$$y = (\overline{x_1} + x_1) \cdot x_3$$

$$y = x_3$$

Principle used: $x + \overline{x} = 1$

$$f = \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y}$$

Apply the Principle: $x + \bar{x} = 1$ to simplify

$$f = \bar{x} \cdot (\bar{y} + y) + x \cdot \bar{y}$$

$$f = \bar{x} + x \cdot \bar{y}$$

How do we simplify further?

$$f = \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y} = \bar{x} \cdot \bar{y} + \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y}$$

Principle used : $x + x = x$

$$\begin{aligned} f &= \bar{x} \cdot \bar{y} + \bar{x} \cdot y + \bar{x} \cdot \bar{y} + x \cdot \bar{y} \\ &= \bar{x} \cdot (\bar{y} + y) + (\bar{x} + x) \cdot \bar{y} = \bar{x} + \bar{y} \end{aligned}$$

Simplify

$$f = \overline{x_1} \cdot \overline{x_2} \cdot \overline{x_3} \cdot x_4 + \overline{x_1} \cdot x_2 \cdot \overline{x_3} \cdot x_4 + x_1 \cdot \overline{x_2} \cdot \overline{x_3} \cdot x_4 + x_1 \cdot x_2 \cdot \overline{x_3} \cdot x_4 + \\ \overline{x_1} \cdot \overline{x_2} \cdot x_3 \cdot x_4 + x_1 \cdot \overline{x_2} \cdot x_3 \cdot x_4$$

Principle: $x + \overline{x} = 1$ and $x + x = x$

Need a systematic and simpler method for applying these two principles

Karnaugh Map (K map) is a popular technique for carrying out simplification

It represents the information in problem in such a way that the two principles become easy to apply

K-map representation of truth table

x	y	min term
0	0	$\overline{x} \cdot \overline{y}$ m0
0	1	$\overline{x} \cdot \underline{y}$ m1
1	0	$\underline{x} \cdot \overline{y}$ m2
1	1	$\underline{x} \cdot \underline{y}$ m3

		y	0	1
x	0		m ₀	m ₁
	1		m ₂	m ₃

x	y	f ₁
0	0	0
0	1	1
1	0	1
1	1	0



		y	0	1
x	0		0	1
	1		1	0

$$f_2 = \sum (0, 2, 3)$$



		y	
		0	1
x	0	1	0
	1	1	1

		y	
		0	1
x	0	1	0
	1	0	1



$$f = \bar{x}.\bar{y} + x.y$$

3-variable K-map representation

x	y	z	min terms	
0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$	m0
0	0	1	$\bar{x} \cdot \bar{y} \cdot z$	m1
0	1	0	$\bar{x} \cdot y \cdot \bar{z}$	m2
0	1	1	$\bar{x} \cdot y \cdot z$	m3
1	0	0	$x \cdot \bar{y} \cdot \bar{z}$	m4
1	0	1	$x \cdot \bar{y} \cdot z$	m5
1	1	0	$x \cdot y \cdot \bar{z}$	m6
1	1	1	$x \cdot y \cdot z$	m7

		yz			
		00	01	11	10
x	0	m ₀	m ₁	m ₃	m ₂
	1	m ₄	m ₅	m ₇	m ₆

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1



		yz			
		00	01	11	10
x	0	0	1	1	0
	1	0	1	1	0

yz		00	01	11	10
x	0	1	0	1	0
	1	0	1	1	0

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

4-variable K-map representation

w	x	y	z	min terms
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
⋮	⋮	⋮	⋮	⋮
1	1	1	0	m_{14}
1	1	1	1	m_{15}



wx \ yz	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}.x.y.z + \overline{w}.x.y.z + \overline{w}.x.\overline{y}.z + \overline{w}.x.y.z$$

$$+ w.x.\overline{y}.z + w.x.y.z + w.x.\overline{y}.z$$

Minimization using Kmap

$$f_2 = \sum (2,3)$$

$$f = x.\bar{y} + x.y$$

$$f = x.(\bar{y} + y)$$

$$f = x$$

A Karnaugh map for a two-variable function f(x, y). The map is a 2x2 grid. The vertical axis is labeled 'x' with values 0 and 1. The horizontal axis is labeled 'y' with values 0 and 1. The cells contain the following values: (0,0) is 0, (0,1) is 0, (1,0) is 1, and (1,1) is 1. A red oval encircles the two cells where x=1, and a red arrow points from the expression x.(y-bar + y) to this oval.

	y	0	1
x	0	0	0
1	1	1	1

Combine terms which differ in only one bit position. As a result, whatever is common remains.

		y	
		0	1
x	0	0	1
	1	0	1

$$f = \bar{x}.y + x.y$$

$$f = (\bar{x} + x).y$$

$$\Rightarrow f = y$$

		y	
		0	1
x	0	1	0
	1	1	0

$$\Rightarrow f = \bar{y}$$

		y	
		0	1
x	0	1	1
	1	0	0

$$\Rightarrow f = \bar{x}$$

Principle: $x + \bar{x} = 1$ and $x + x = x$

$$f_2 = \sum (0, 2, 3)$$

	y	0	1
x	0	0	1
	1	1	1

$$f = x.\bar{y} + x.y + \bar{x}.y$$

$$\begin{aligned} f &= x.(\bar{y} + y) + \bar{x}.y \\ &= x + \bar{x}.y \end{aligned}$$

$$\begin{aligned} f &= x + \bar{x}.y + x.y \\ &= x + (\bar{x} + x).y \\ &= x + y \end{aligned}$$

The idea is to cover all the 1's with as few and as simple terms as possible

3-variable minimization

x \ yz	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$x.z$

$y.z$

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.z + x.y.z + x.\bar{y}.z$$

$$f = \bar{x}.\bar{y}.\bar{z} + y.z + x.z$$

3-variable minimization

x \ yz	00	01	11	10
0	1	0	0	1
1	0	1	1	0

$x.z$

$\bar{x}.\bar{z}$

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.\bar{z} + x.y.z + x.\bar{y}.z$$

$$f = \bar{x}.\bar{z} + x.z$$

3-variable minimization

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$x.\bar{y}$$

$$x.y$$





$$f = x.\bar{y}.\bar{z} + x.\bar{y}.z + x.y.z + x.y.\bar{z}$$

$$f = x.\bar{y} + x.y$$

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$x$$

$$f = x.(\bar{y} + y) = x$$

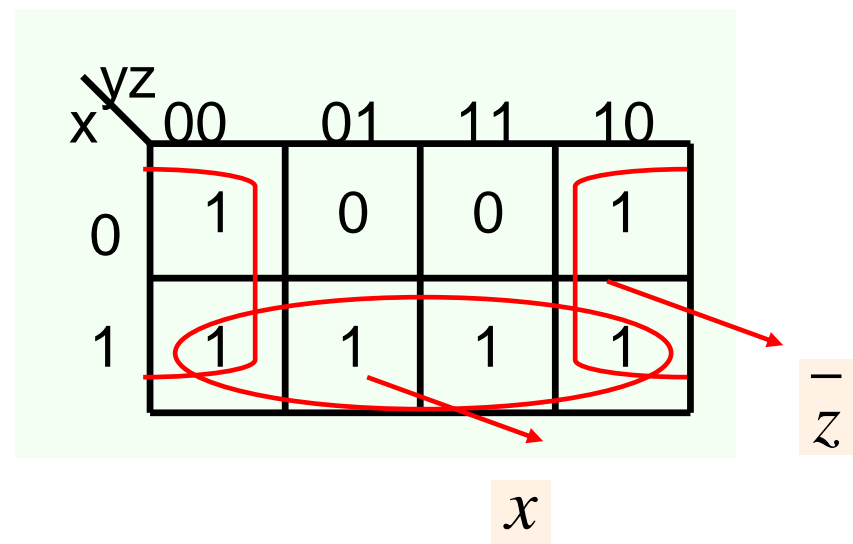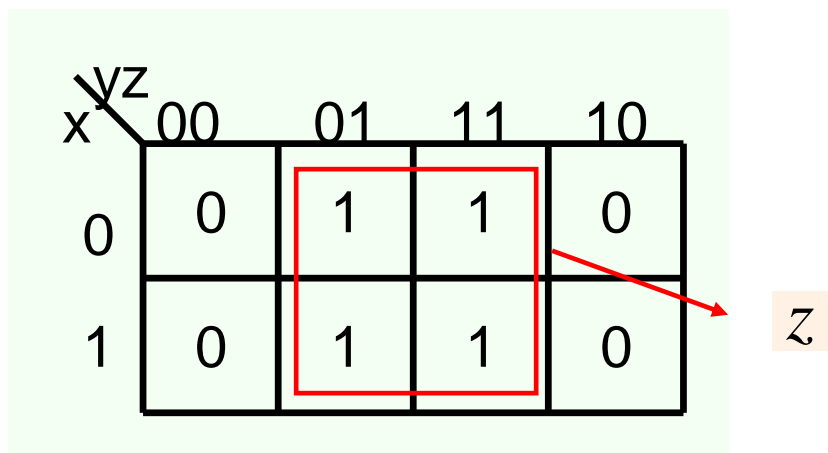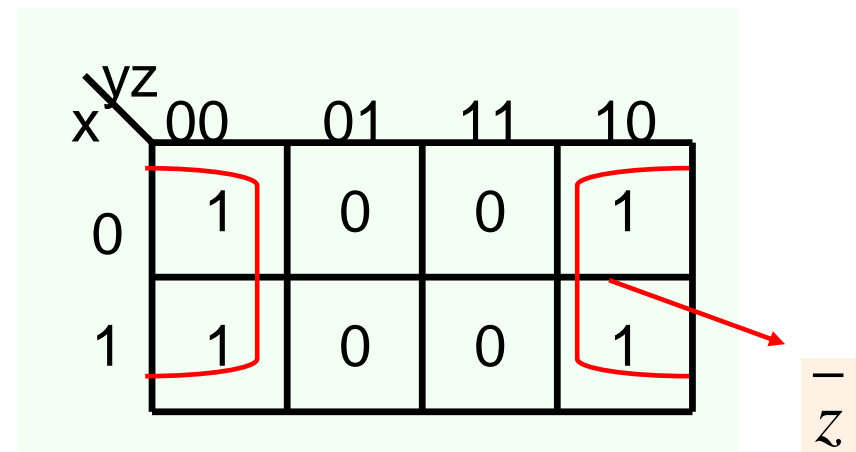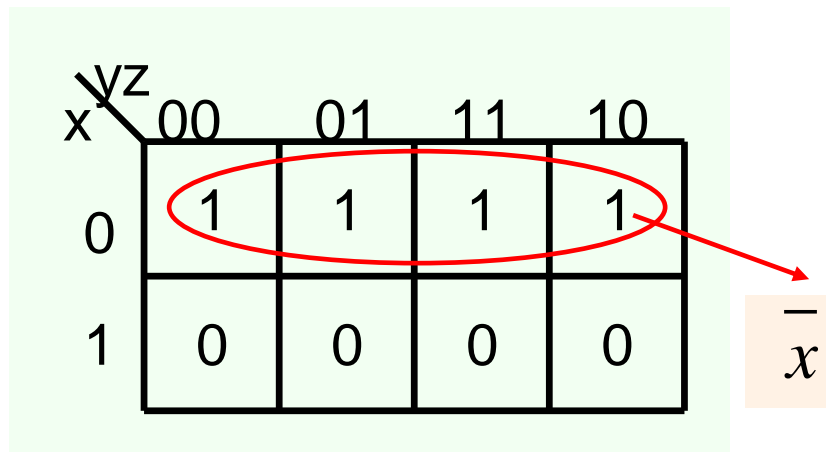

$$f = x + \bar{z}$$

Can we do this ?

x \ yz	00	01	11	10
0	0	0	0	0
1	0	1	1	0

Note that each encirclement should represent a single product term. In this case it does not.

$$\begin{aligned}f &= x.\bar{y}.\bar{z} + x.\bar{y}.z + x.y.\bar{z} \\ &= x.\bar{y} + x.z\end{aligned}$$

We do not get a single product term. In general we cannot make groups of 3 terms.

Can we use kmap with the following ordering of variables?

x \ yz	00	01	10	11
0	0	0	0	0
1	0	1	1	0

Can we combine these two terms into a single term ?

$$\begin{aligned}f &= x.\bar{y}.z + x.y.\bar{z} \\ &= x.(\bar{y}.z + y.\bar{z})\end{aligned}$$

Note that no simplification is possible. Kmap requires information to be represented


$x \backslash yz$	00	01	10	11
0	0	1	0	1
1	0	0	0	0

These two terms can be combined into a single term but it is not easy to show that on the diagram.

$$\begin{aligned}
 f &= \bar{x}.\bar{y}.z + \bar{x}.y.z \\
 &= \bar{x}.(\bar{y} + y).z = \bar{x}.z
 \end{aligned}$$

Kmap requires information to be represented in such a way that it is easy to apply the principle $x + \bar{x} = 1$

4-variable minimization

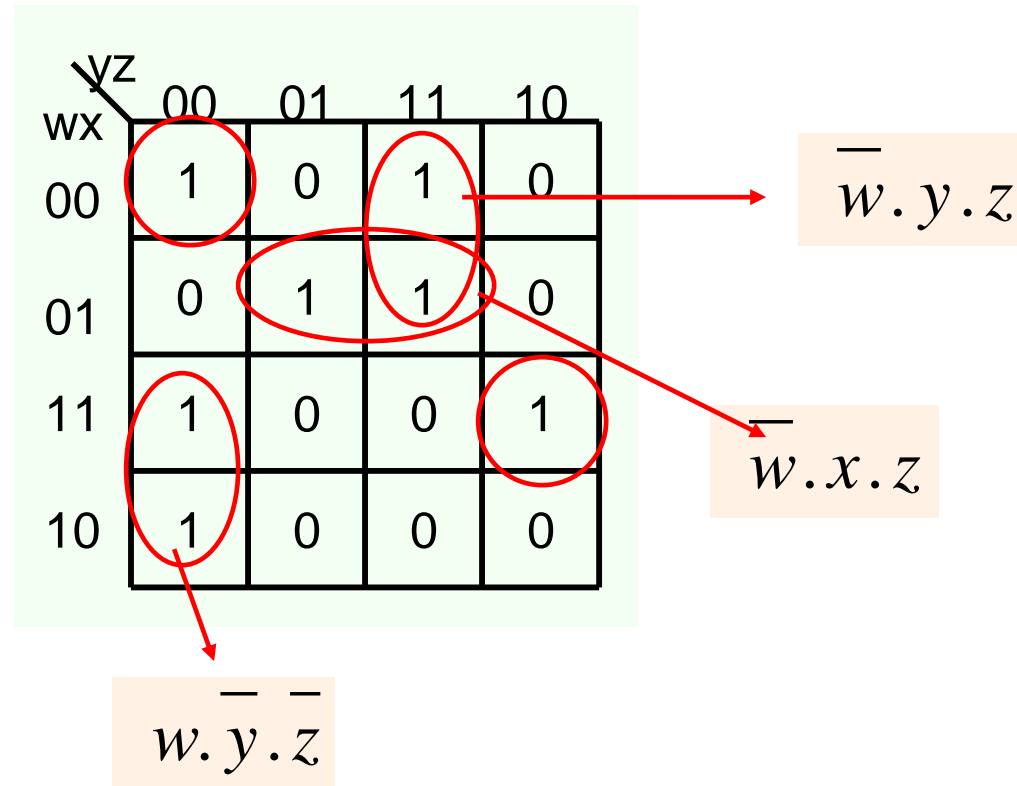

$$f = \overline{w}.y.z + \overline{w}.x.z + w.\overline{y}.\overline{z} + \overline{w}.\overline{x}.\overline{y}.\overline{z} + w.x.y.\overline{z}$$

But is this the simplest expression ?


		yz			
		00	01	11	10
wx	00	1	0	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	0	0	0

$$w \cdot x \cdot \bar{y} \cdot \bar{z} + w \cdot x \cdot y \cdot \bar{z} = w \cdot x \cdot \bar{z}$$

		yz			
		00	01	11	10
wx	00	1	0	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	0	0	0

$$w \cdot \bar{x} \cdot \bar{y} \cdot \bar{z} + w \cdot \bar{x} \cdot y \cdot \bar{z} = \bar{x} \cdot \bar{y} \cdot \bar{z}$$

4-variable minimization

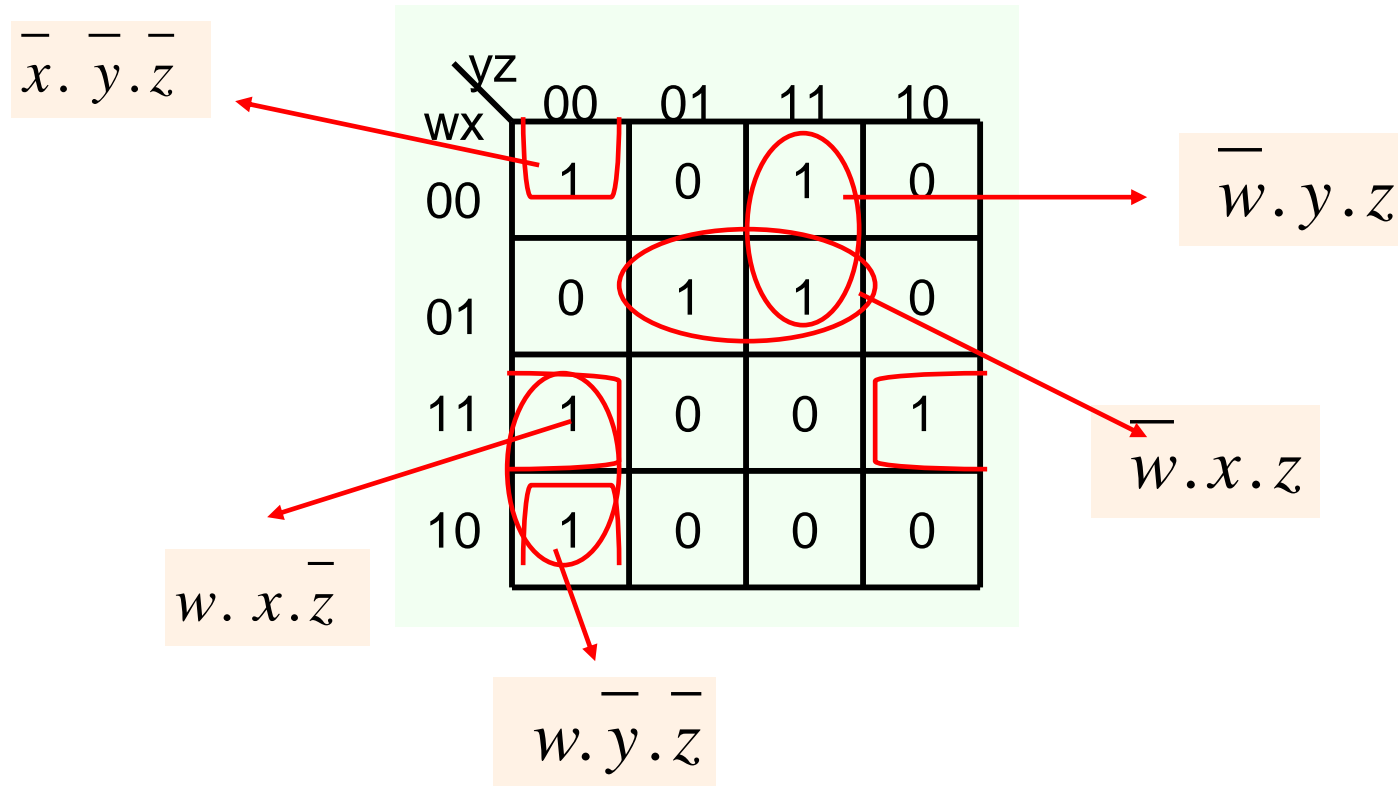

$$f = \bar{w}.y.z + \bar{w}.x.z + w.\bar{y}.\bar{z} + w.x.\bar{z} + \bar{x}.\bar{y}.\bar{z}$$

Is this the best that we can do ?

Cover the 1's with minimum number of terms

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}.y.z + \overline{w}.x.z +$$

$$w.\overline{y}.\overline{z} + w.x.\overline{z} + \overline{x}.\overline{y}.\overline{z}$$

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}.y.z + \overline{w}.x.z +$$

$$w.x.\overline{z} + \overline{x}.\overline{y}.\overline{z}$$

4-variable minimization



wx \ yz	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	0	0	1

$$f = \overline{w}.x.\overline{y} + \overline{w}.x.z + \overline{w}.\overline{y}.z$$

wx \ yz	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	0	0	1

$$f = \overline{w}.x.\overline{y} + \overline{w}.x.z + x.\overline{y}.z$$

Groups of 4

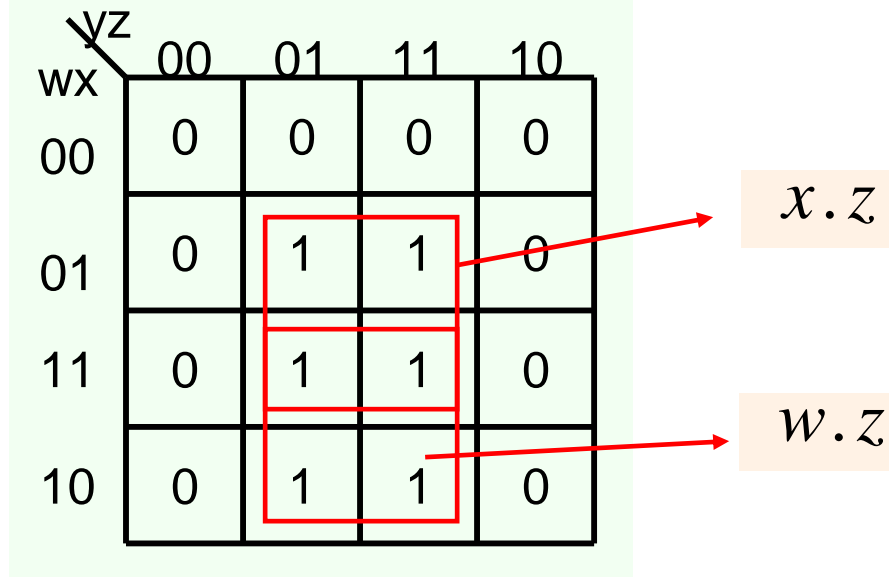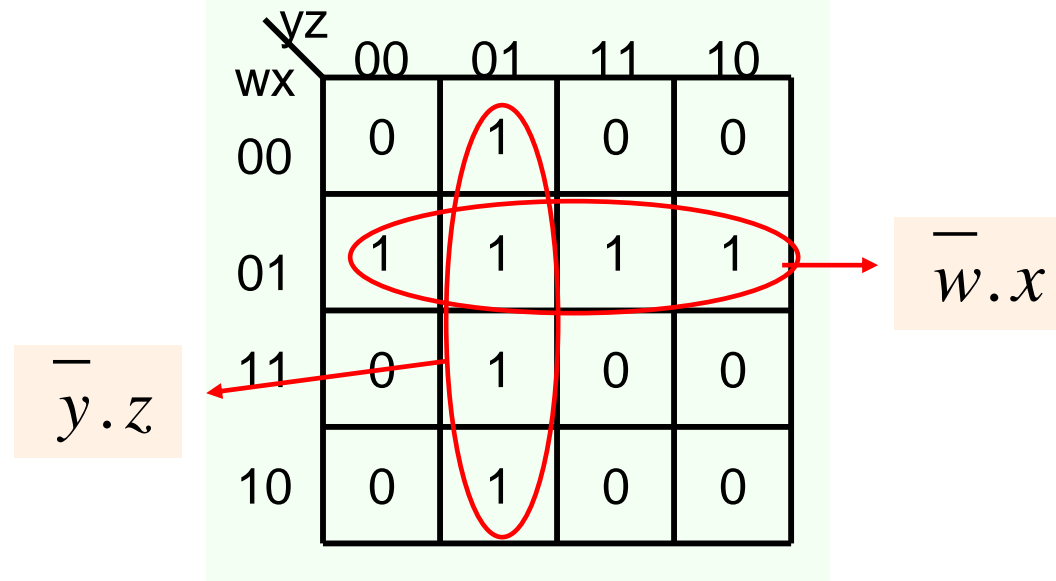

wx \ yz	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

$\overline{x} \cdot z$

wx \ yz	00	01	11	10
00	0	1	1	0
01	0	0	0	0
11	0	0	0	0
10	0	1	1	0

$\overline{x} \cdot z$

wx \ yz	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

$\overline{\overline{x}} \cdot \overline{\overline{z}}$

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	0	0	0
11	0	0	0	0
10	1	0	1	0

??

Groups of 8

wx \ yz	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

z

wx \ yz	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

x

wx \ yz	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

\bar{z}

wx \ yz	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	0	0	0	0
10	1	1	1	1


\bar{x}

Examples

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	1	1
11	1	1	1	1
10	0	0	0	1

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	0	1
11	1	1	1	1
10	0	0	0	1

Don't care terms

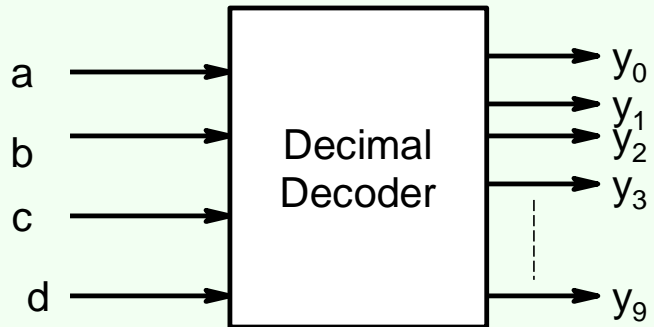

Y_3

cd \ ab	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	x	x	x	x
10	0	0	x	x

$$y_3 = \overline{a}.\overline{b}.c.d$$

[illegible]

Don't care terms can be chosen as 0 or 1. Depending on the problem, we can choose the don't care term as 1 and use it to obtain a simpler Boolean expression

Y_3

cd \ ab	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	x	x	x	x
10	0	0	x	x

$$y_3 = \bar{b}.c.d$$

Don't care terms should only be included in encirclements if it helps in obtaining a larger grouping or smaller number of groups.

Minimization of Product of Sum Terms using Kmap

x \ y	0	1
	0	1
0	0	1
1	1	1

$$\begin{aligned}f &= x + \bar{x}.y + x.y \\&= x + (\bar{x} + x).y \\&= x + y\end{aligned}$$

x \ y	0	1
	0	1
0	0	1
1	1	1

$$f = x + y$$

x \ y	0	1
	0	1
0	0	1
1	0	1

$$f = y$$

		y	
		0	1
x	0	1	0
	1	1	0

$$\Rightarrow f = \bar{y}$$

		y	
		0	1
x	0	1	1
	1	0	0

$$\Rightarrow f = \bar{x}$$


$$\bar{x} + z$$

		yz			
		00	01	11	10
x	0	1	0	0	1
	1	0	1	1	0

$$x + \bar{z}$$

$$f = (\bar{x} + z) \cdot (x + \bar{z})$$
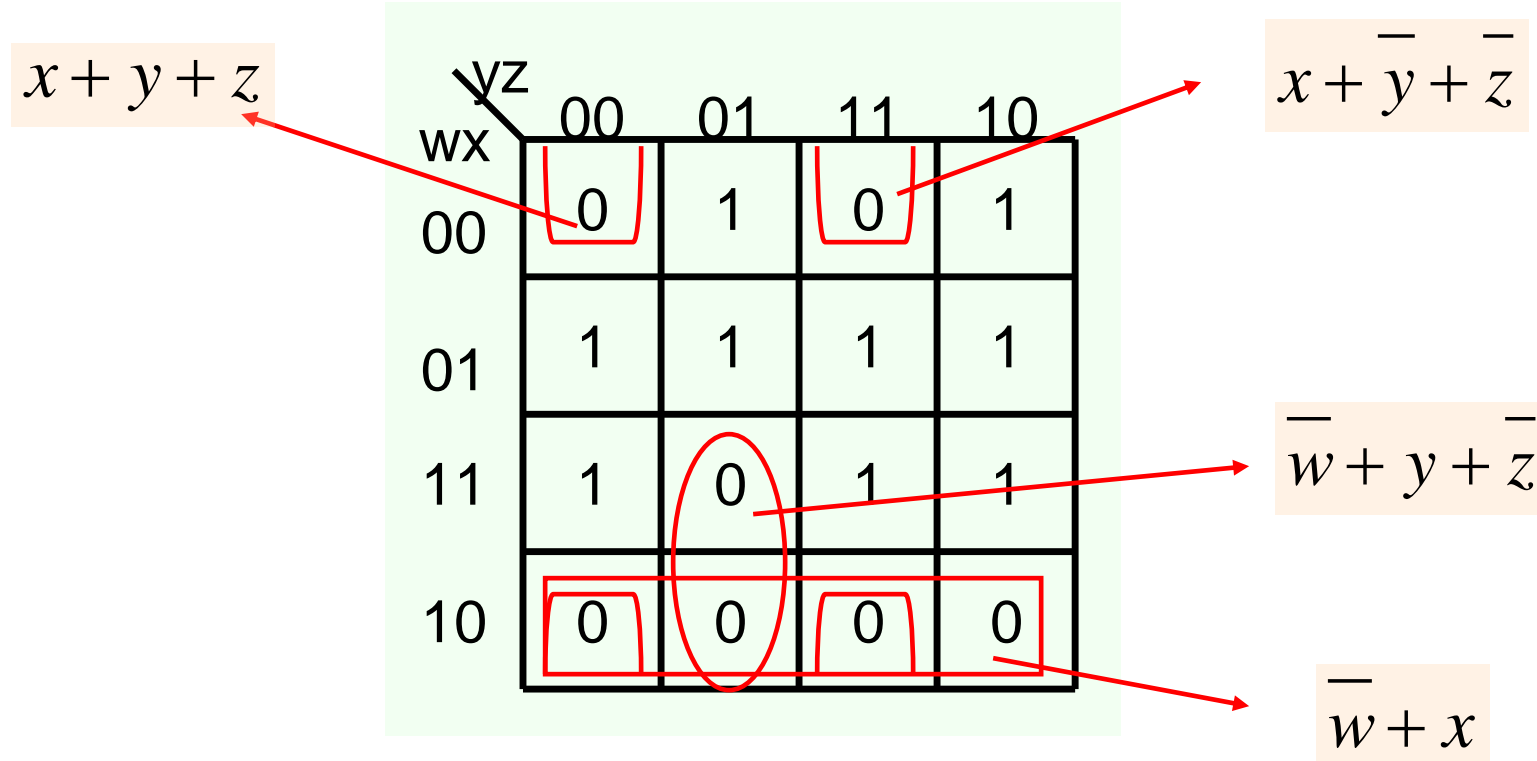
$$\Rightarrow f = \bar{x} \cdot \bar{z} + x \cdot z$$



$$f = (x + y + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{w} + y + \bar{z}) \cdot (\bar{w} + x)$$


Example

Obtain the minimized PoS by suitably using don't care terms


wx \ yz	00	01	11	10
00	1	x	0	1
01	1	0	1	1
11	0	x	1	1
10	1	x	1	x

$$f = (x + w + \bar{z}).(\bar{x} + \bar{w} + y).(y + \bar{z})$$

Adder/Subtractor


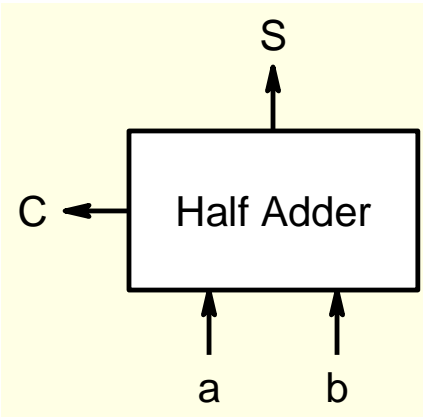


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

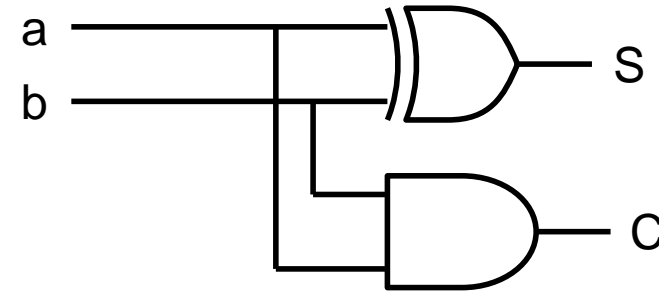

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

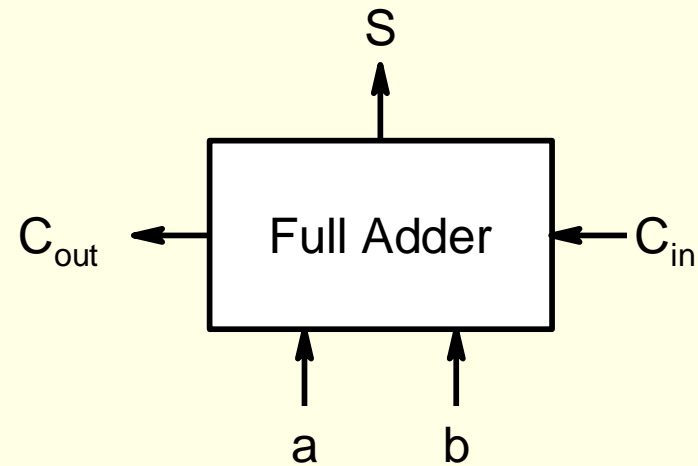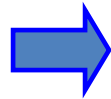$\overset{1}{1}11$
 $\underline{110}$
 1111



a	b	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in}; C_{out} = a.b + a.c_{in} + b.c_{in}$$

$$S = \overline{a}.\overline{b}.c_{in} + \overline{a}.b.\overline{c_{in}} + a.\overline{b}.\overline{c_{in}} + a.b.c_{in}$$


$$S = C_{in} \oplus (a \oplus b)$$

$$C_{out} = a.b + a.C_{in} + b.C_{in}$$
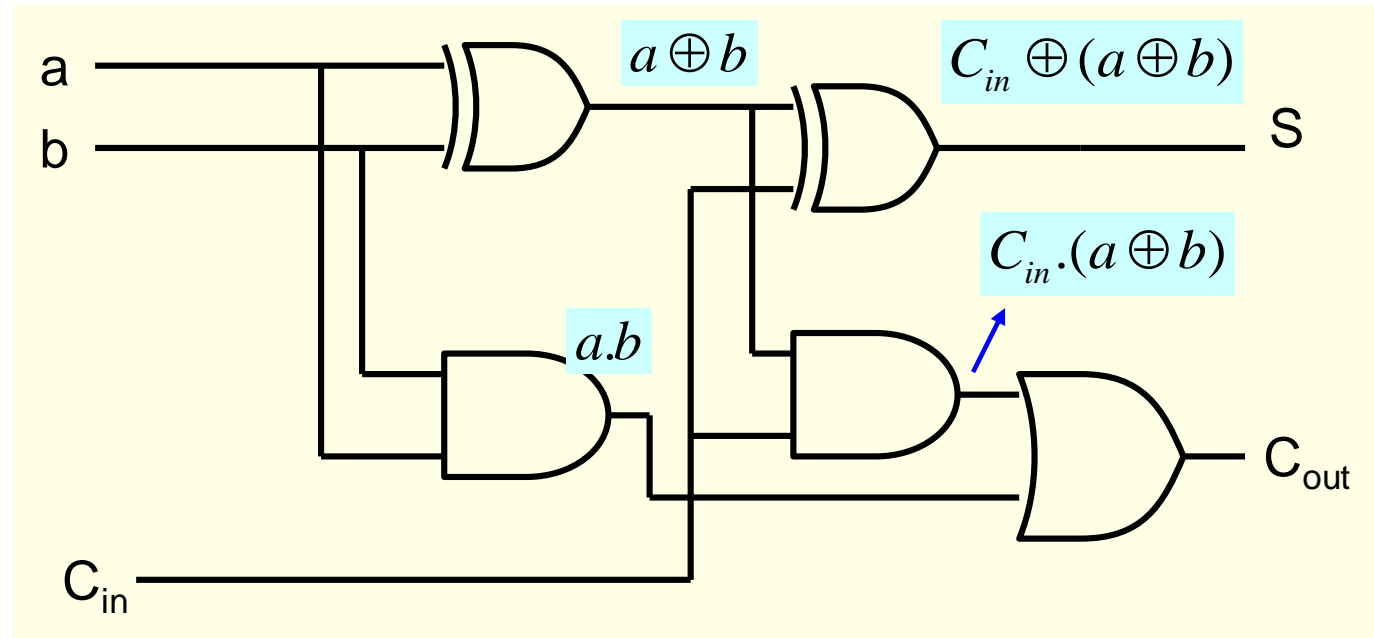
$$C_{out} = C_{in} (a.\overline{b} + \overline{a}.b) + a.b = C_{in} \cdot (a \oplus b) + a.b$$




4-bit Adder

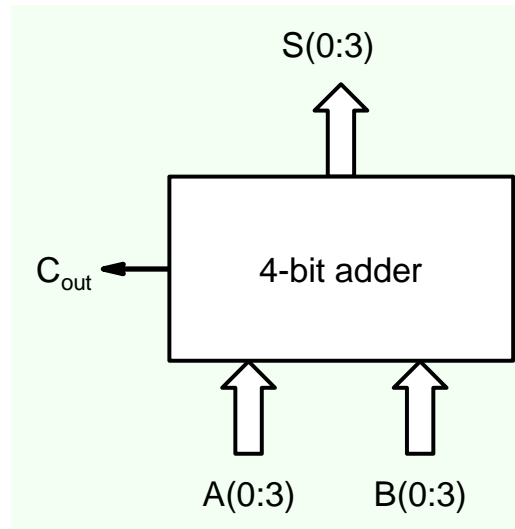

$A_3A_2A_1A_0$	$B_3B_2B_1B_0$	$S_3S_2S_1S_0$	C_{out}
0000	0000	0000	1
0000	0001	0001	0
0001	0000	0001	0
⋮	⋮	⋮	⋮
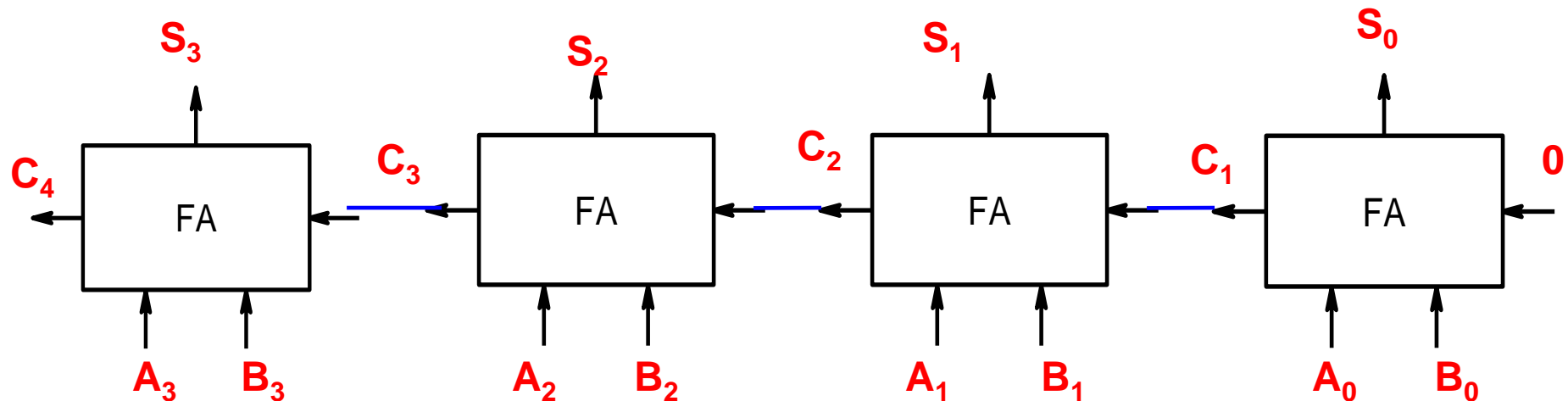
$$\begin{array}{r} C_3 C_2 C_1 \\ A_3 A_2 A_1 A_0 \\ B_3 B_2 B_1 B_0 \\ \hline C_4 S_3 S_2 S_1 S_0 \end{array}$$




Ripple Carry Adder (20 gate circuit)

Subtraction

$$A - B = A + 2\text{'s complement of } B$$




$$A - B = A + 1\text{'s complement of } B + 1$$

$$A - B = A + \overline{B} + 1$$

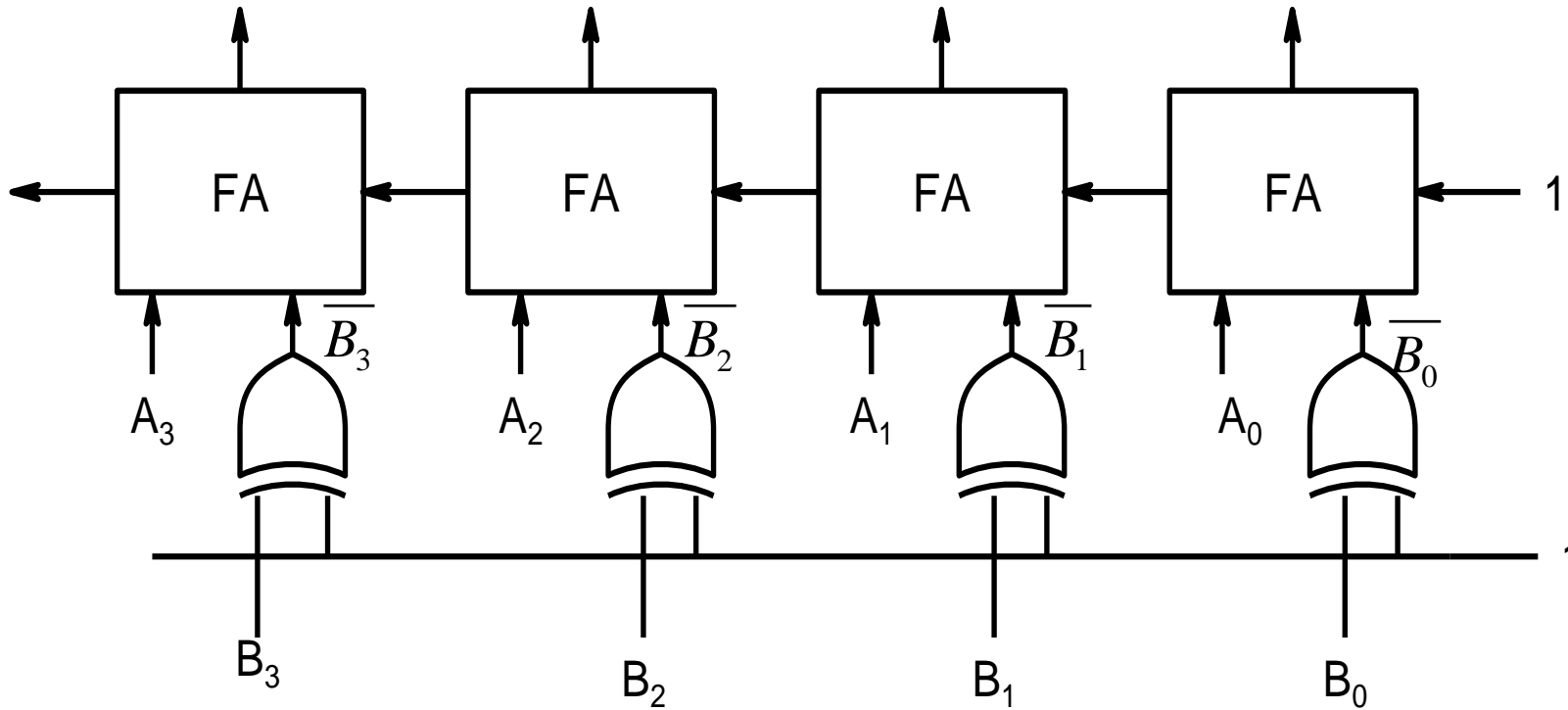


One needs add a circuit for predicting errors resulting from overflow

Adder/Subtractor

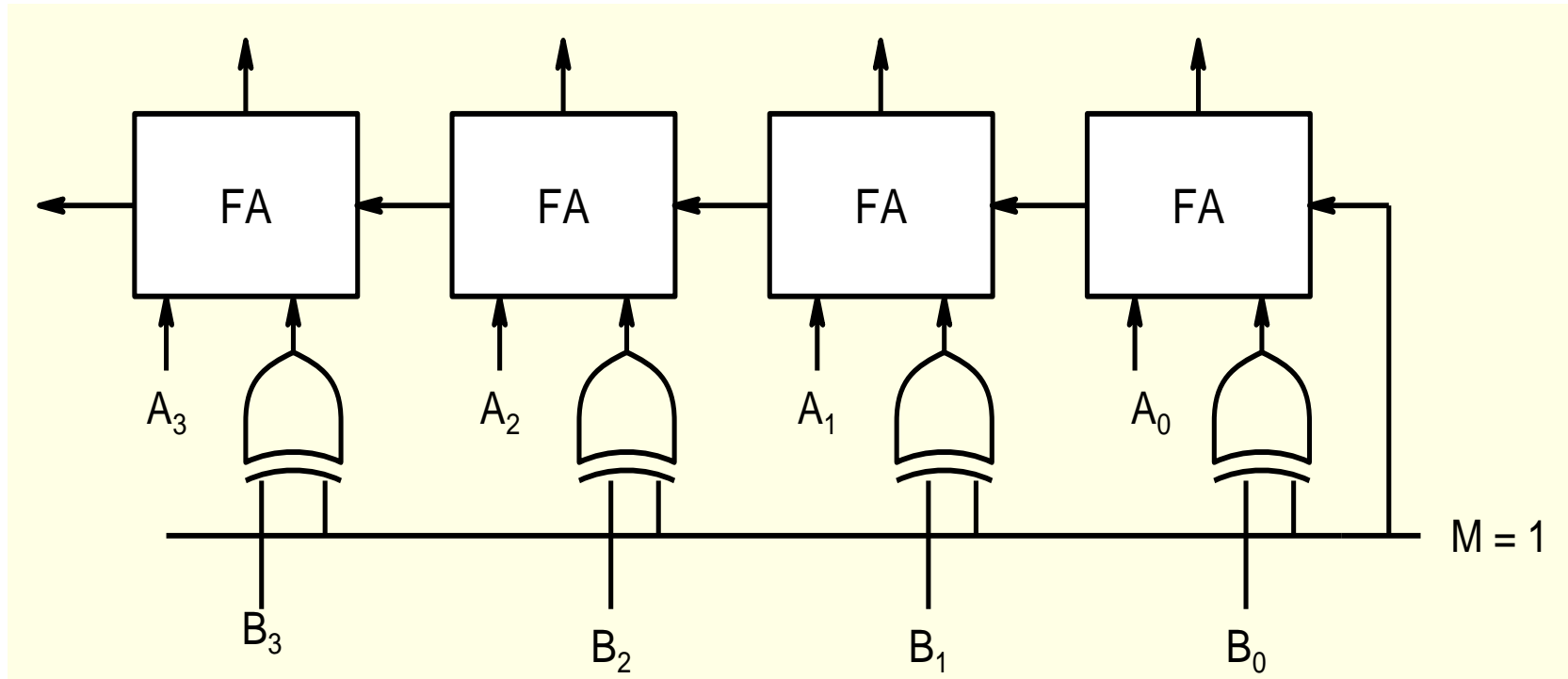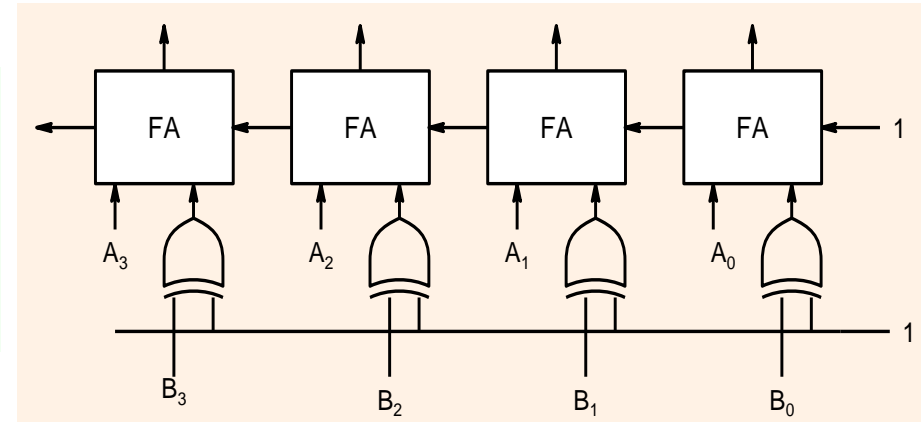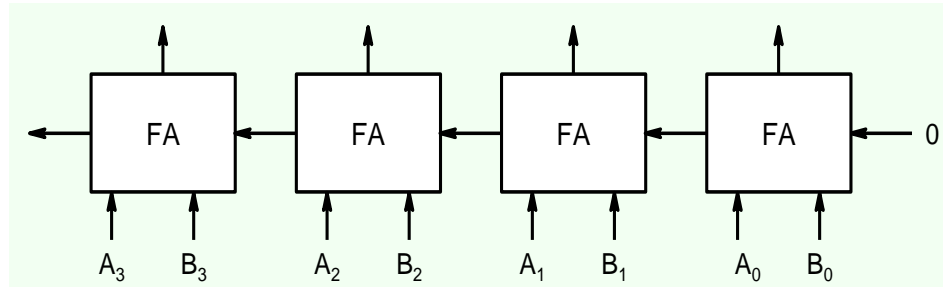


Digital Circuits

Combinational Circuits

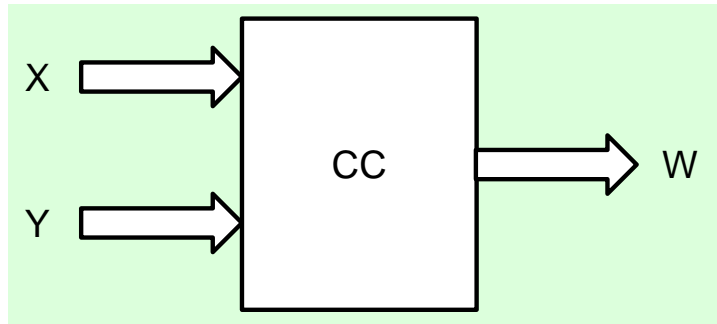


Output is determined by current values of inputs only.

Sequential Circuits

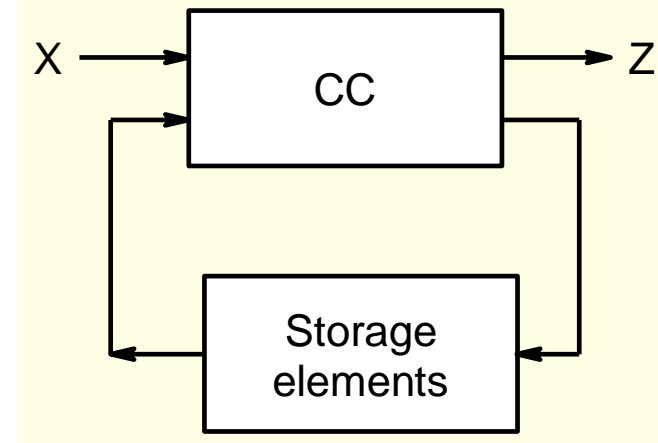

Output is determined in general by current values of inputs and past values of inputs/outputs as well.

NOR SR Latch

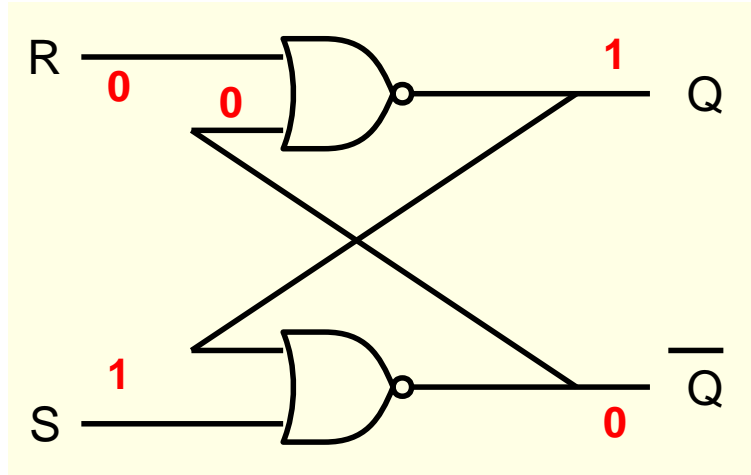


$Q = 1; \overline{Q} = 0$ Set State

$Q = 0; \overline{Q} = 1$ Reset State

S	R	Q	\overline{Q}	State
1	0	1	0	SET

NOR SR Latch

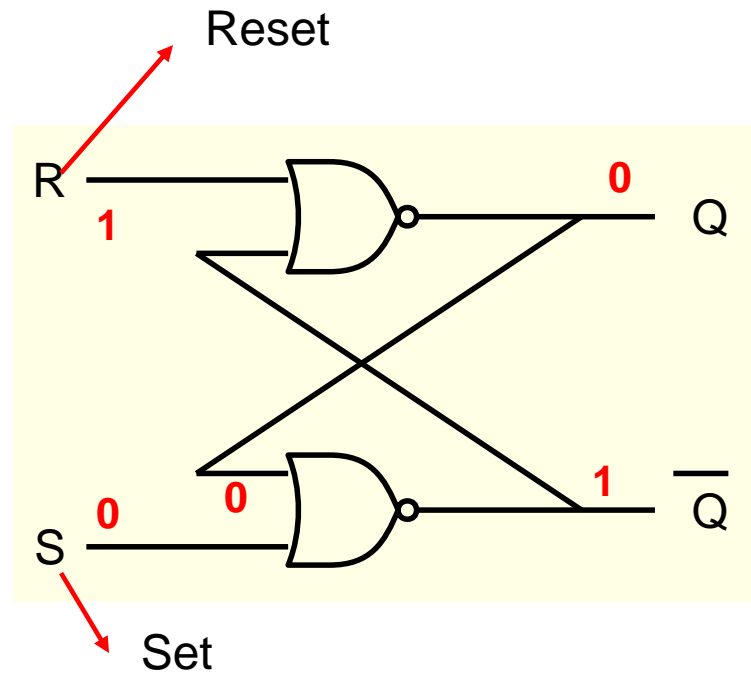


$Q = 1; \bar{Q} = 0$ Set State


$Q = 0; \bar{Q} = 1$ Reset State

S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET

HOLD State



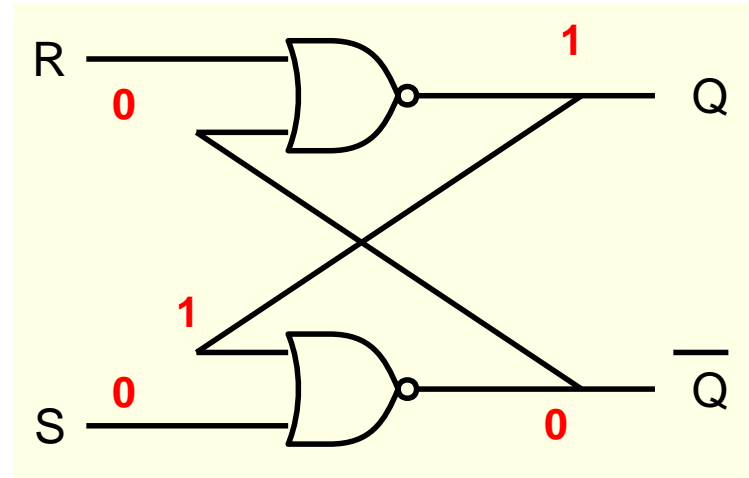


S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID



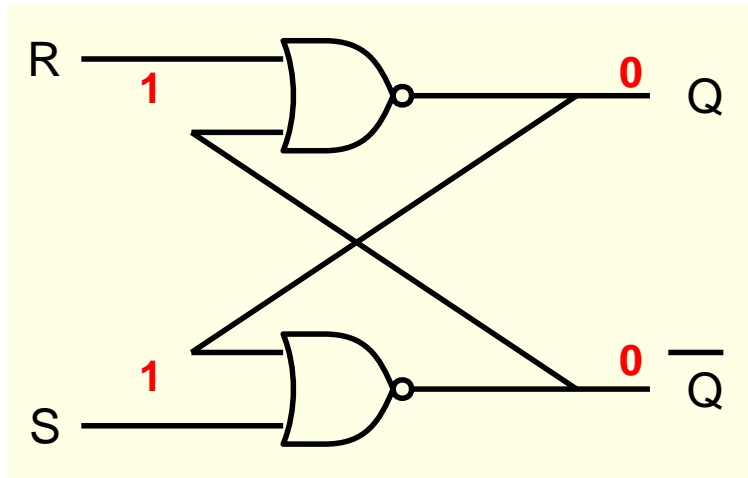


Both the outputs are well defined and 0. the first problem is that we do not get complementary output.

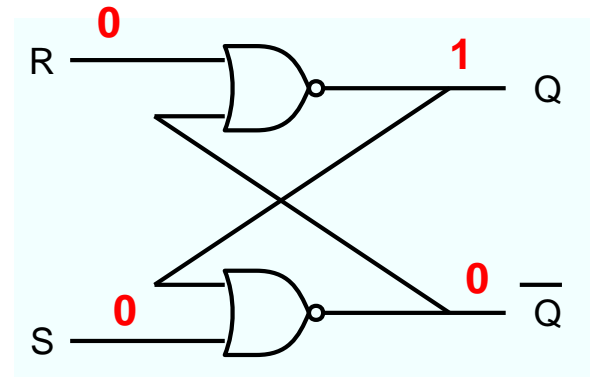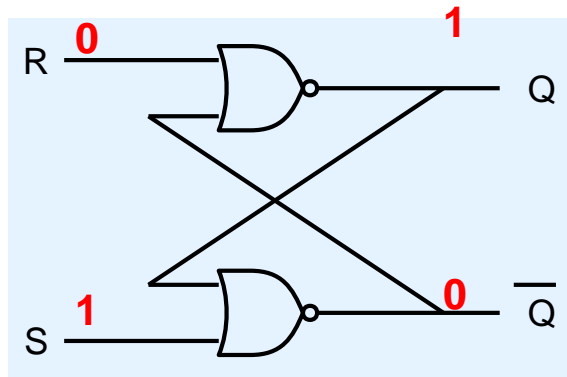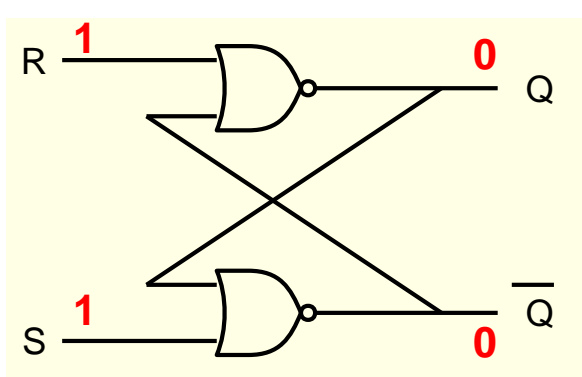A more serious problem occurs when we switch the latch to the hold state by changing RS from $11 \rightarrow 00$. Suppose the inputs do not change simultaneously and we get the situation $11 \rightarrow 01^* \rightarrow 00$






Q = 1

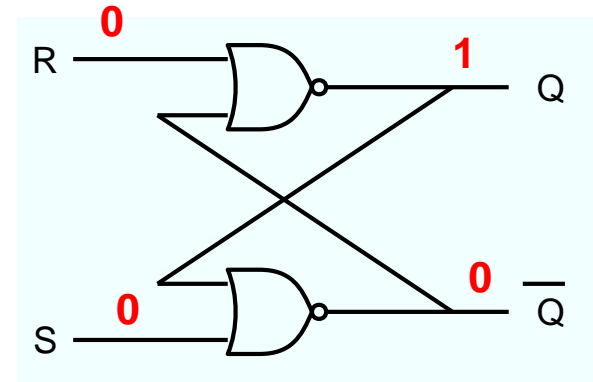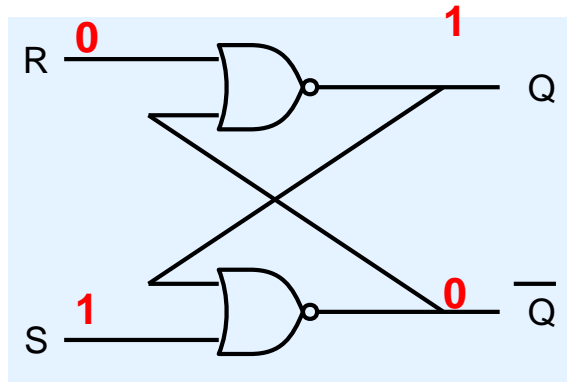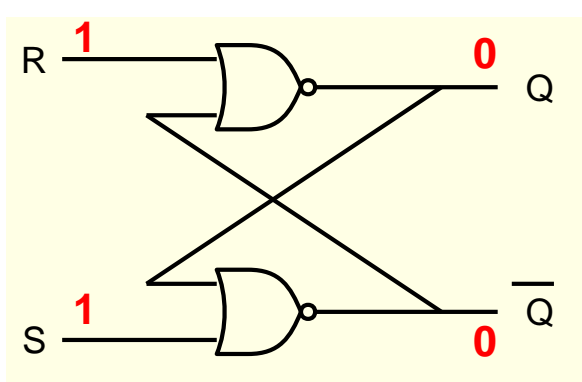

Q = 1

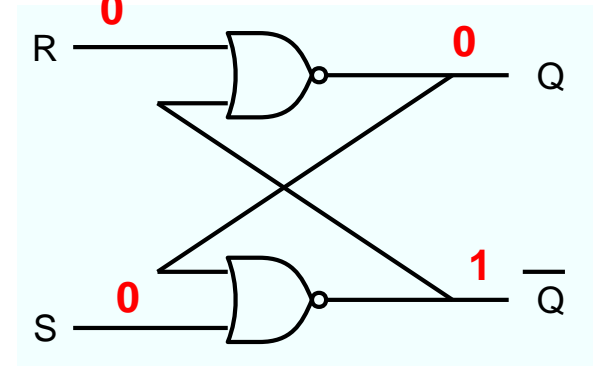
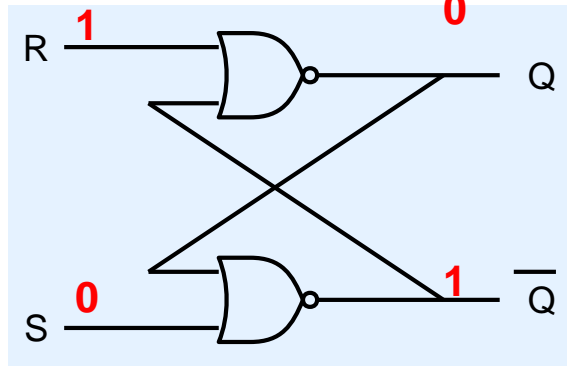
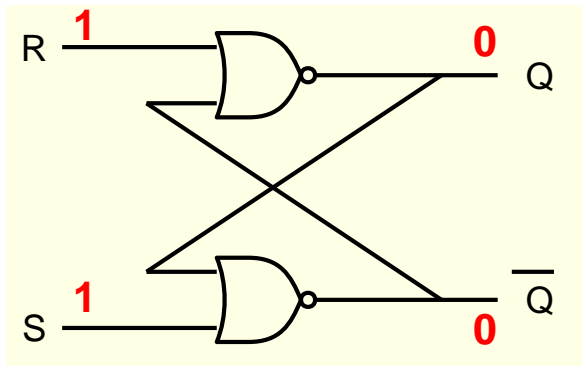
Suppose the inputs change as $RS = 11 \rightarrow 10^* \rightarrow 00$



Q = 0

So although output is well defined when we apply $RS = 11$, it becomes unpredictable once we switch the latch to hold state by applying $RS = 00$. That is why $RS = 11$ is not used as an input combination.

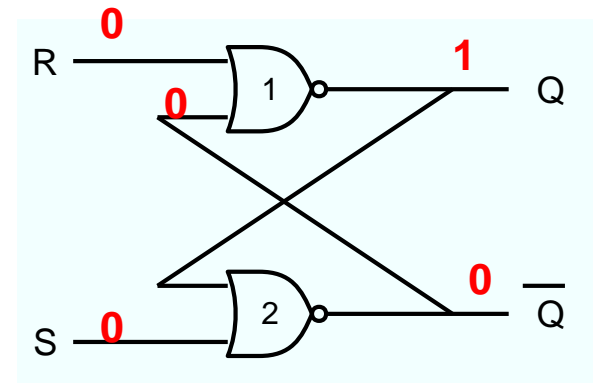
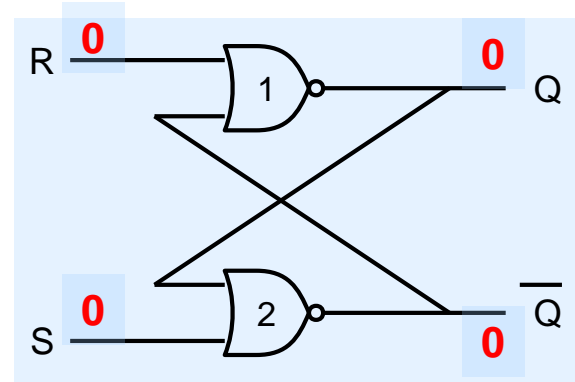
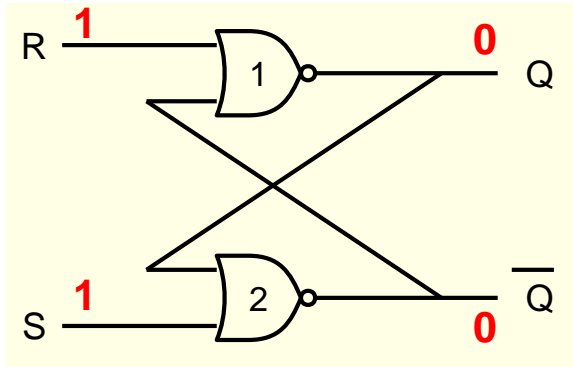
The error can occur also due to unequal gate delays.



Q = 1

Suppose gate-1 is faster

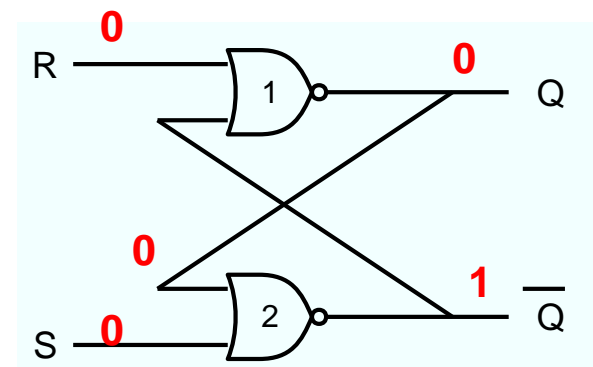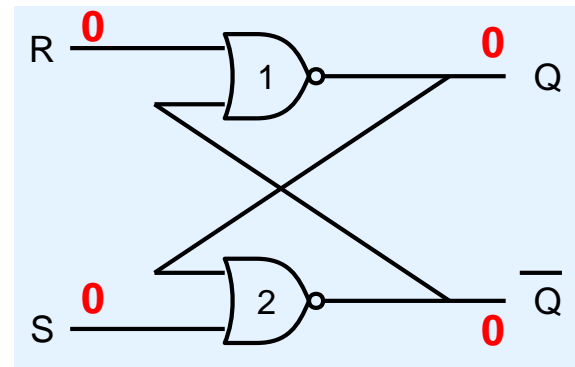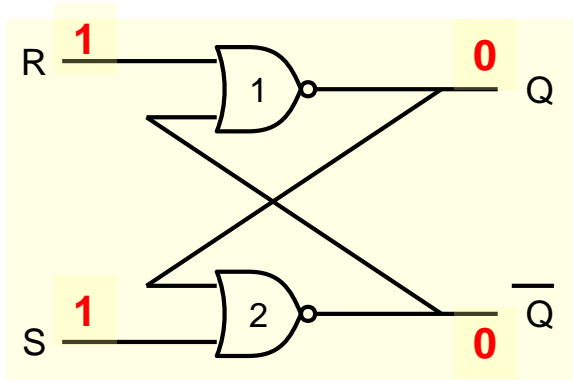
On the other hand suppose that gate-2 is faster.



Q = 0


Again the output is unpredictable in general

NAND Latch

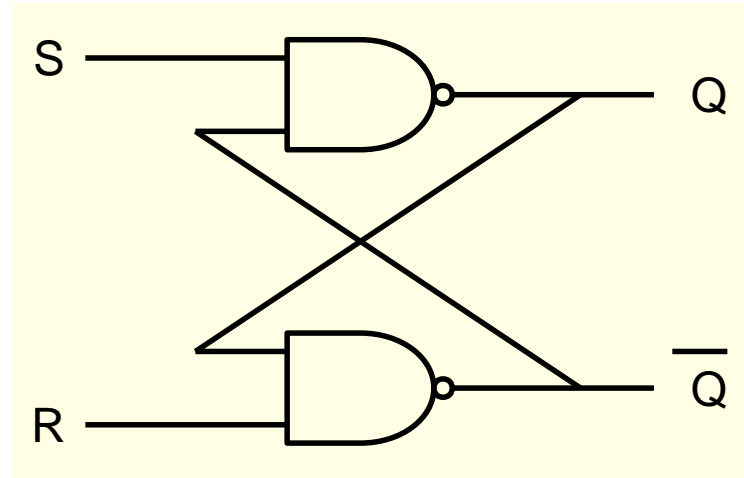


S	R	Q	\overline{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	HOLD
0	0	1	1	INVALID

D latch


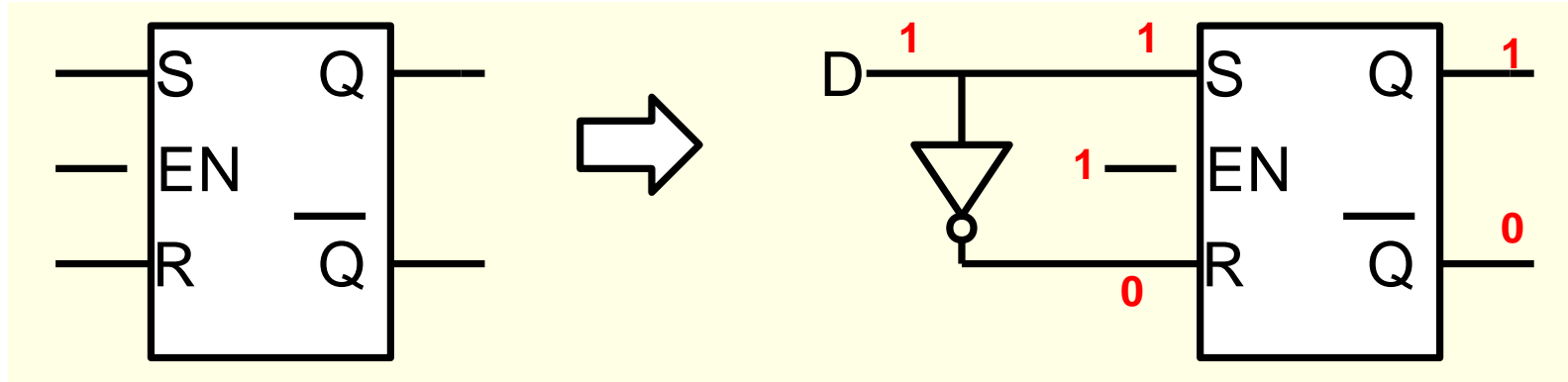


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid


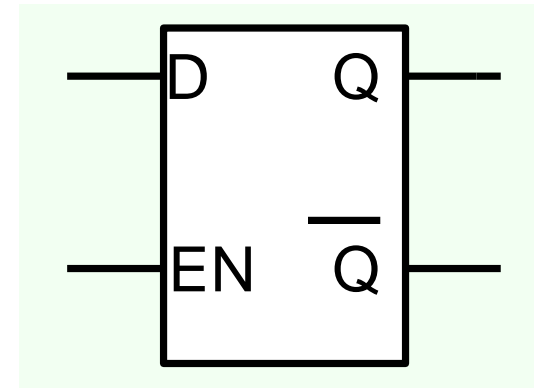


If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state



Synchronous Sequential Circuits

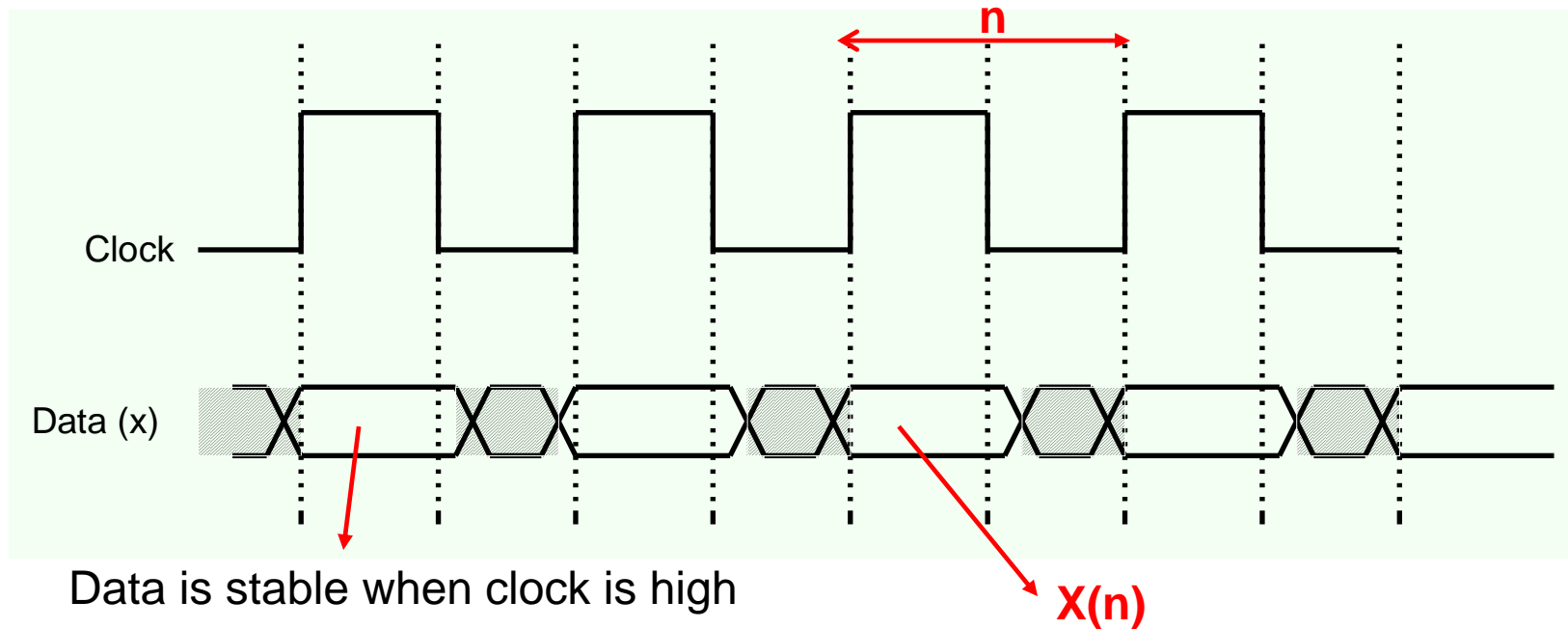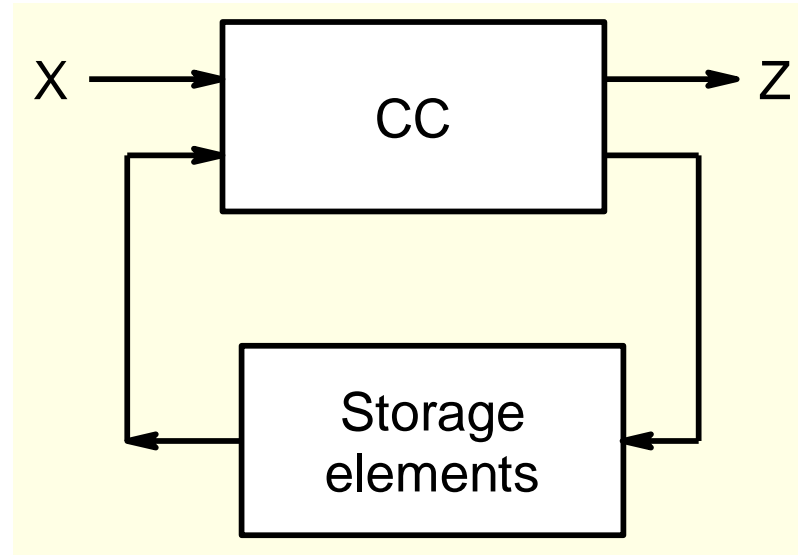


Example

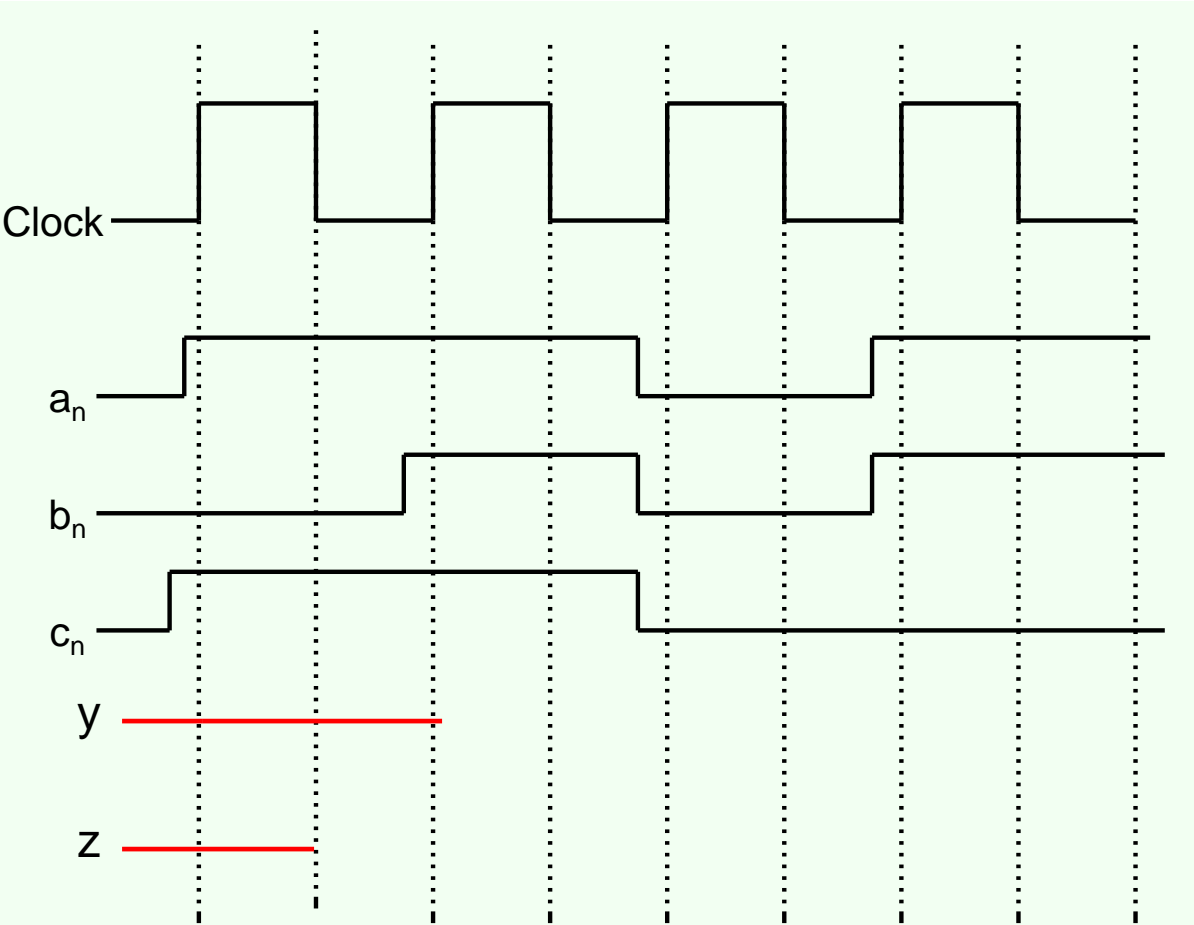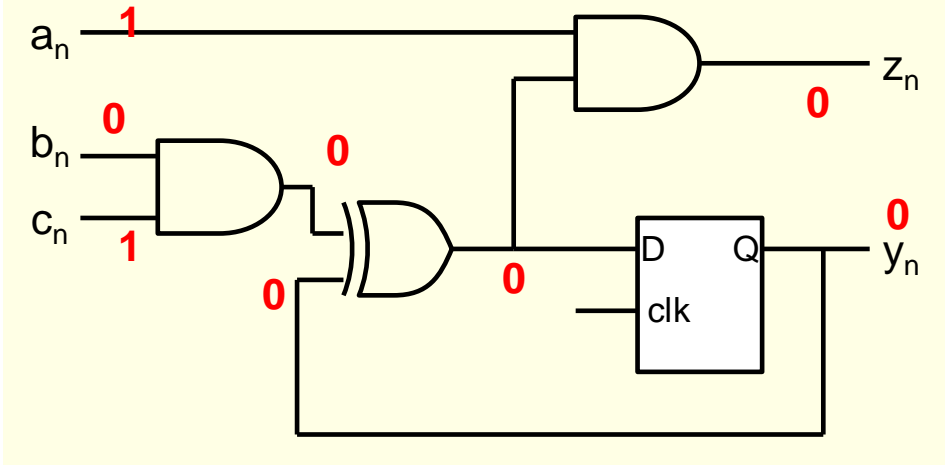


Example

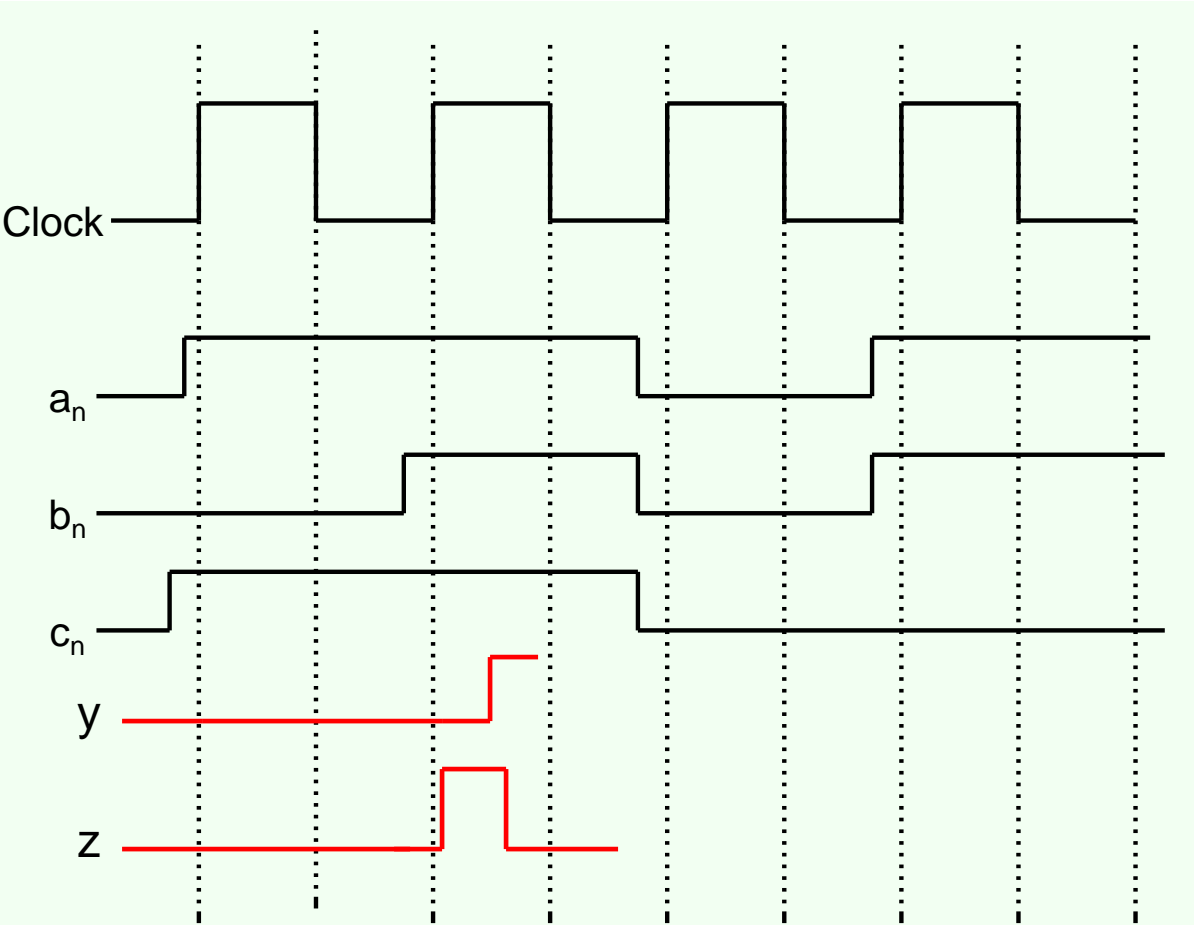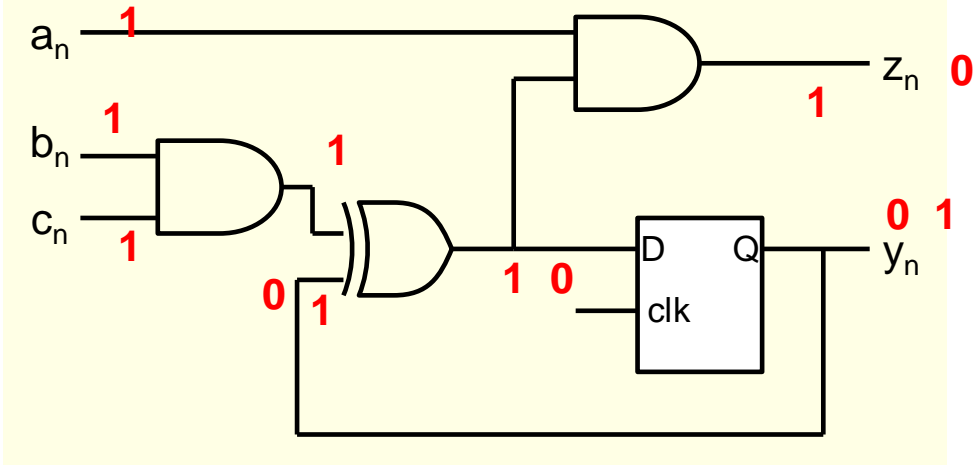



Problem with Latch

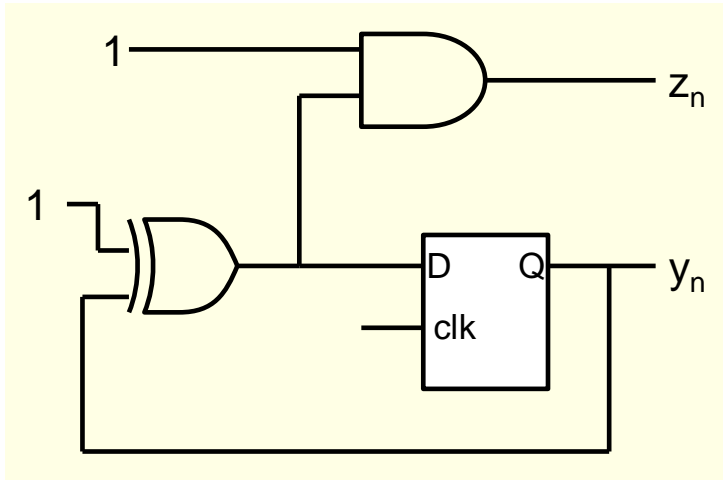

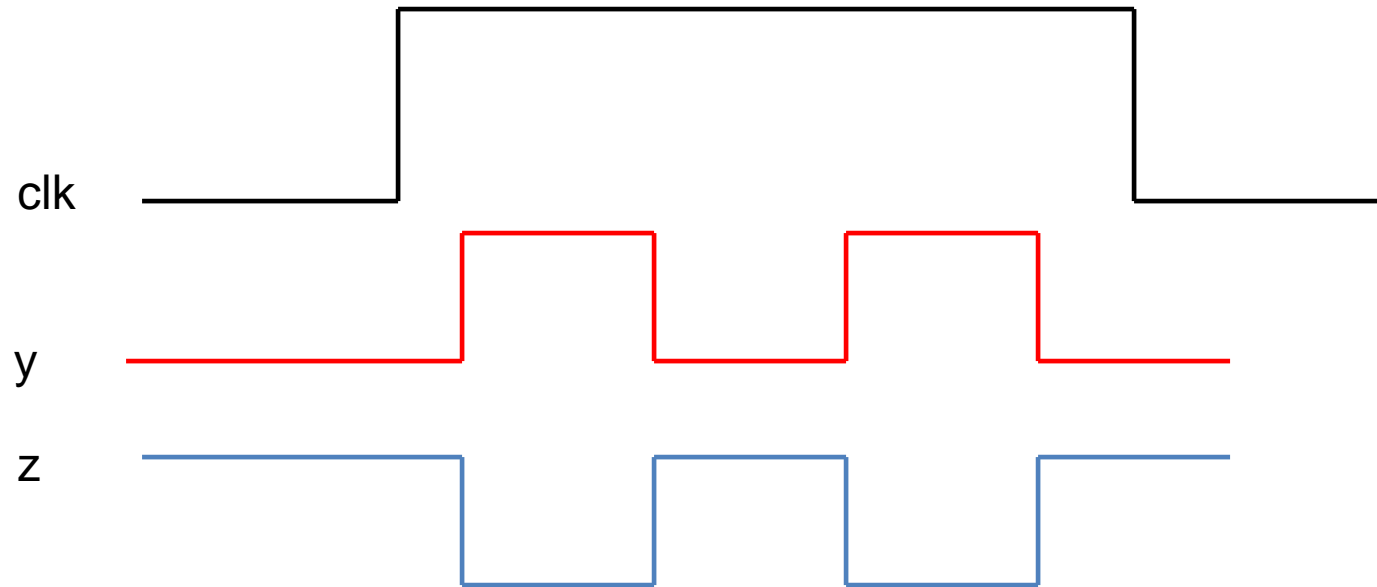Circuits are designed with the idea there would be single change in output or memory state in single clock cycle.





Edge Triggered Latch or Flip-flop


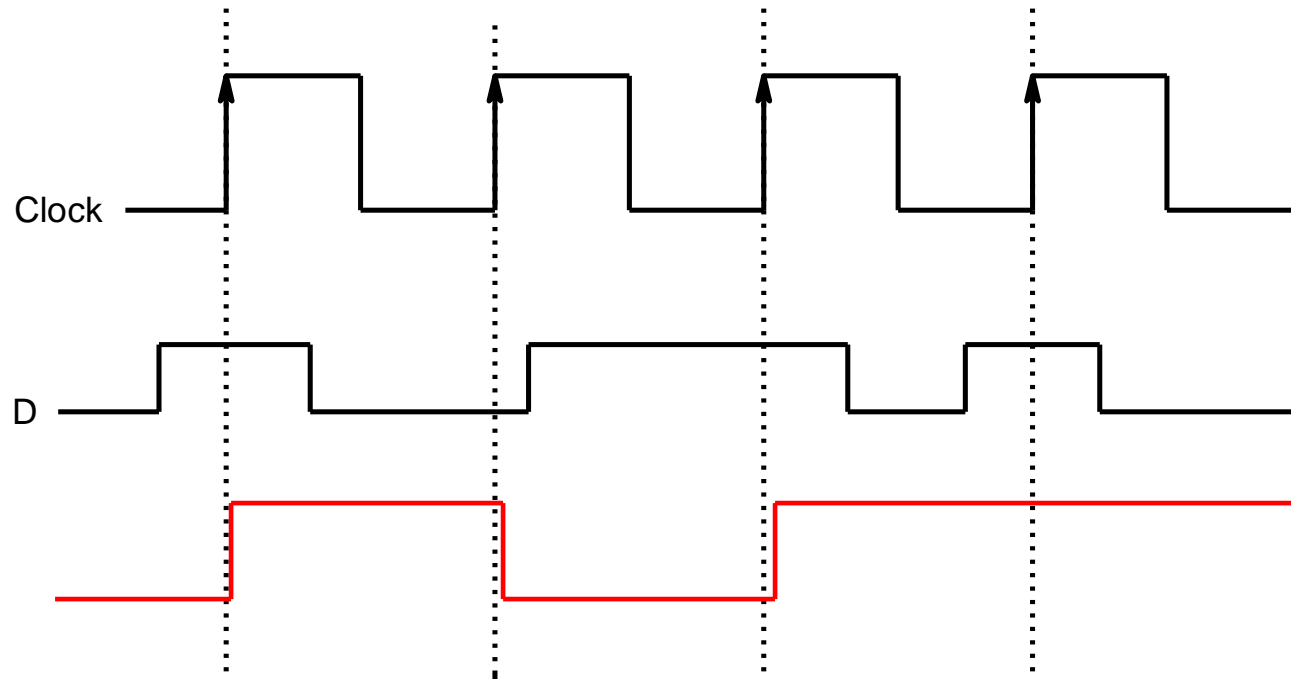
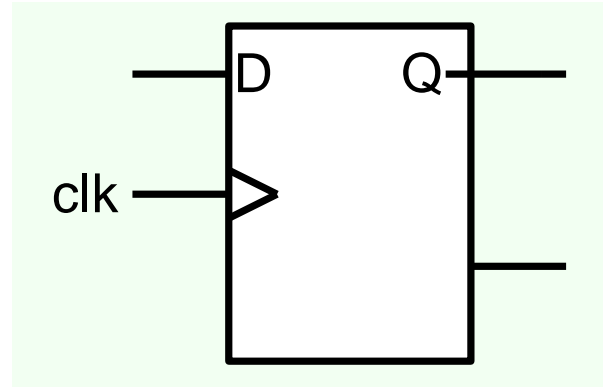


Positive edge triggered flipflop

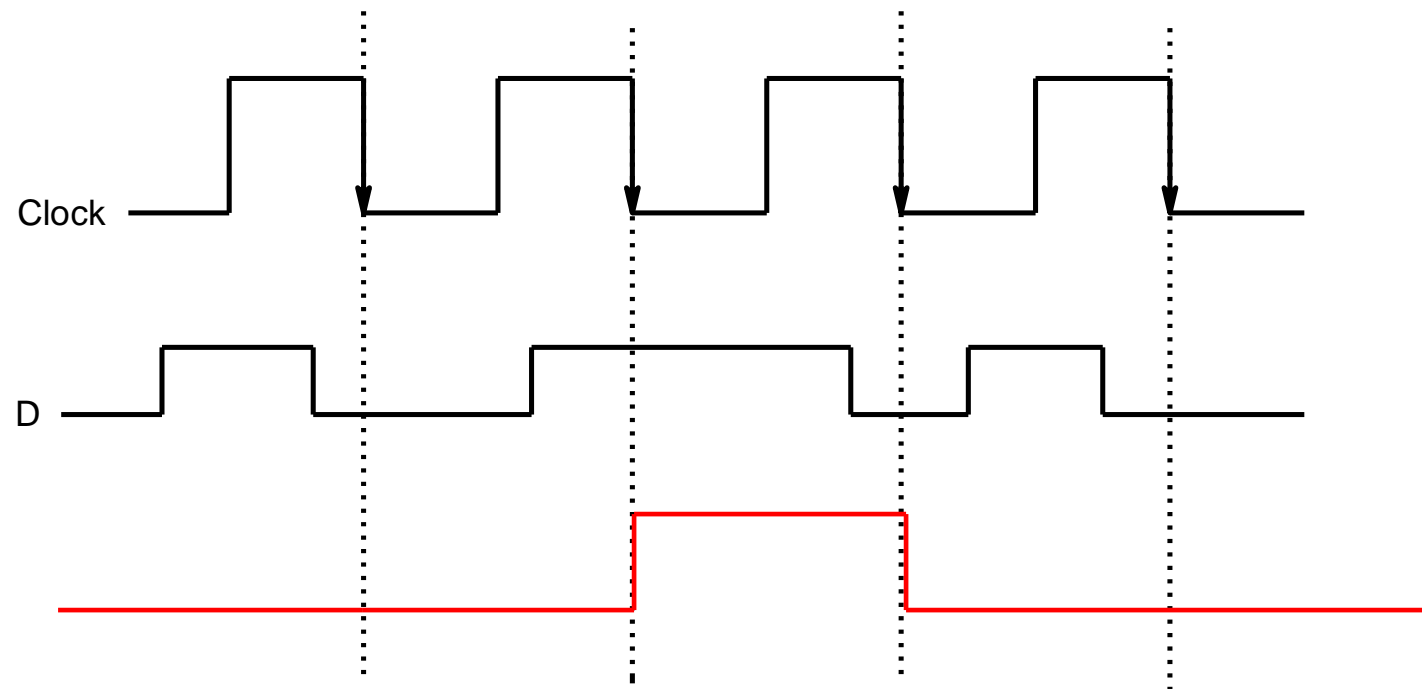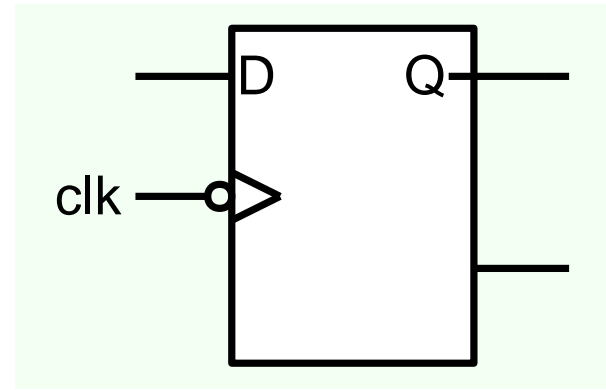Negative Edge Triggered Latch or Flip-flop




Master-Slave D Flip-flop

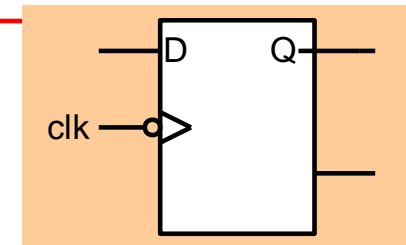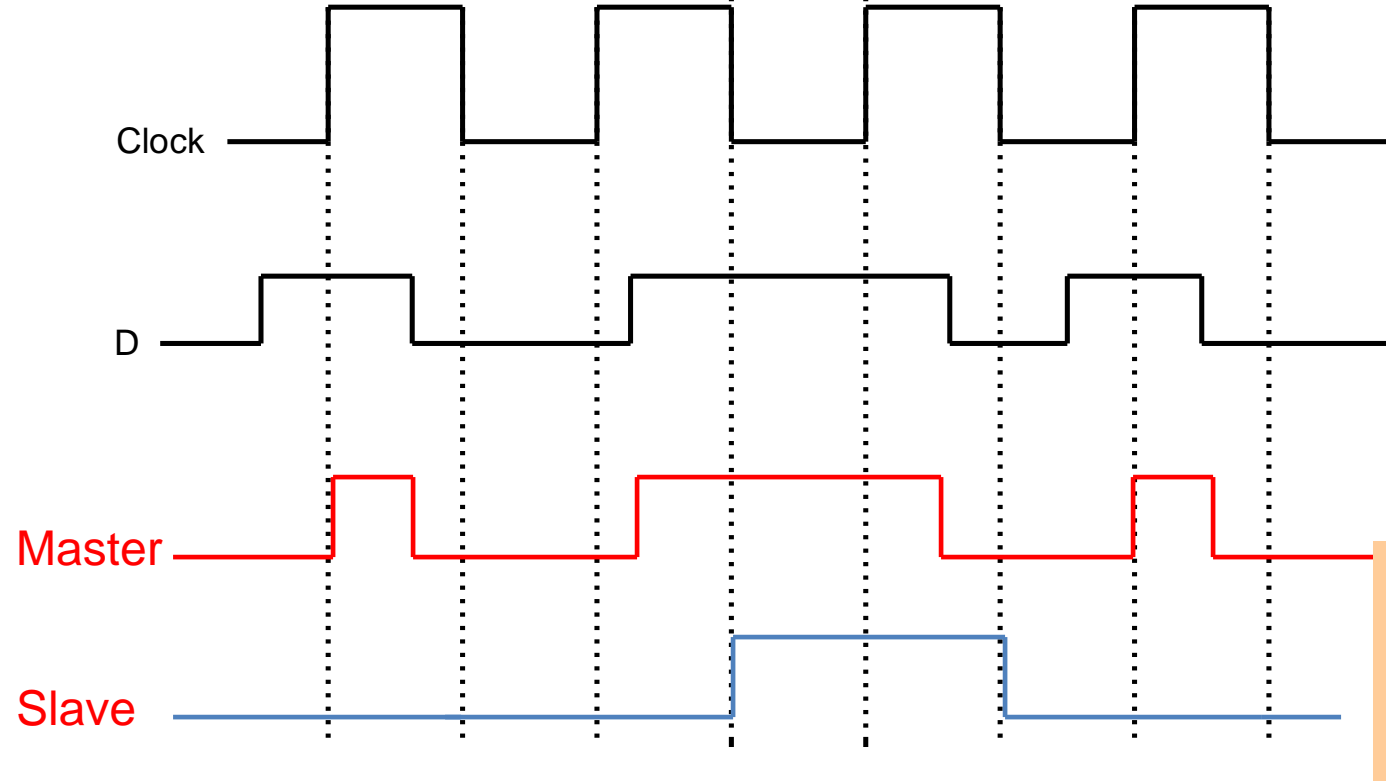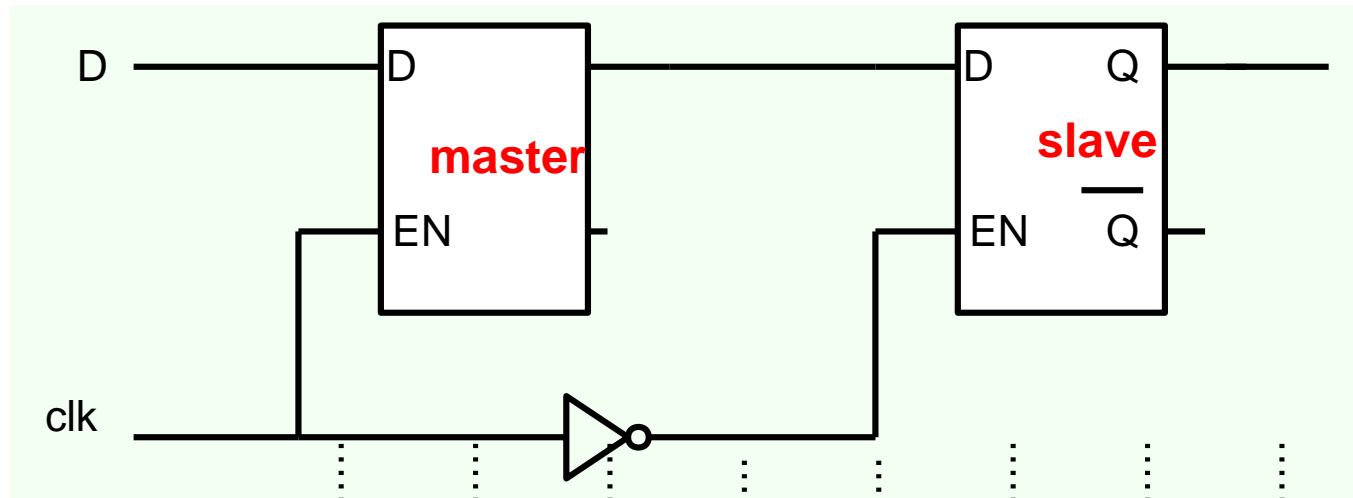

Characteristic table

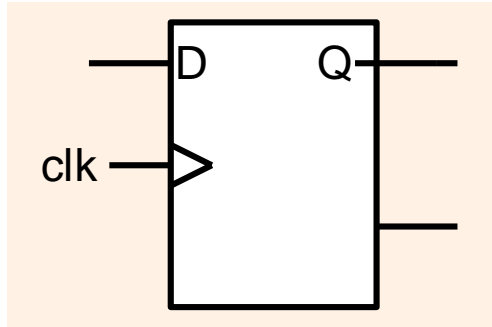
Given a input and the present state of the flip-flop, what is the next state of the flip-flop



Inputs (D)	Q(t+1)
0	0
1	1

$$Q(t+1) = D$$

JK Flip-flop

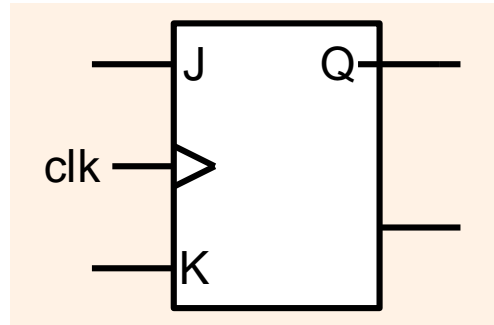


Inputs J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

$$Q(t+1) = \overline{Q(t)}.J + Q(t).\overline{K}$$

→Characteristic equation

Toggle or T Flip-flop

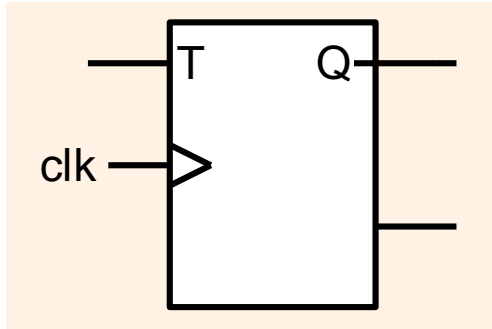

Inputs (T)	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$


$$Q(t+1) = \overline{Q(t)}.T + Q(t).\overline{T}$$

Excitation Table

What inputs are required to effect a particular state change

Inputs		
$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0


Excitation Table

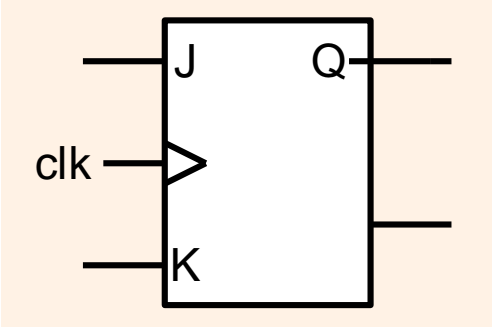

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

Inputs

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

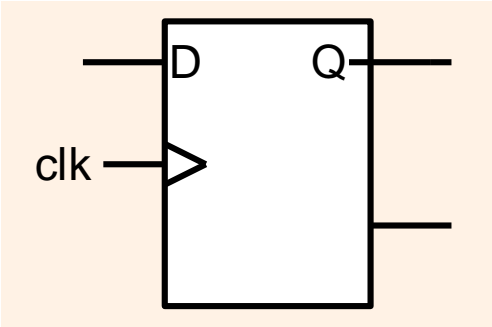


D	Q(t+1)
0	0
1	1

Inputs

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Convert a D FF to JK FF

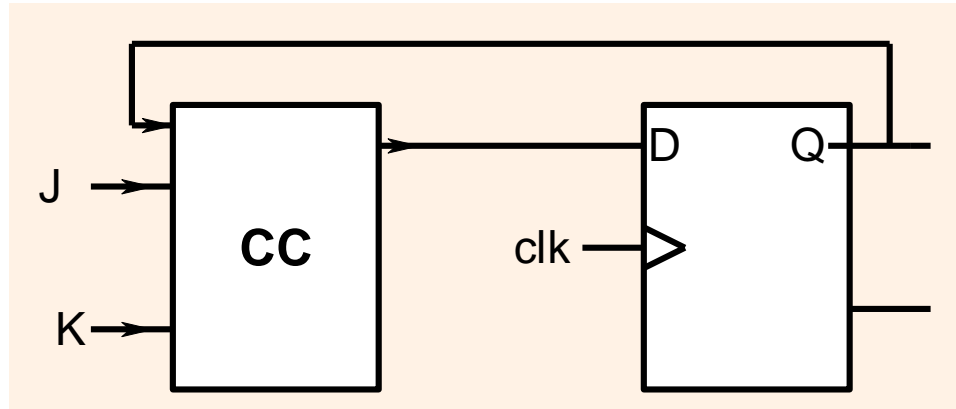

J	K	Q(t+1)	D
0	0	Q(t)	Q(t)
0	1	0	0
1	0	1	1
1	1	$\overline{Q(t)}$	$\overline{Q(t)}$

Q \ JK	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$D = \overline{Q}.J + Q.\overline{K}$$

